

Načrtovanje digitalnih sistemov

Digitalni elektronski sistemi 2024/25

Andrej Trost



Načrtovanje digitalnih sistemov

- delovanje digitalnega sistema postopoma razdelimo na podrobneje določene naloge: od zgoraj navzdol (**top-down**)
- vezje razdelimo na bloke (komponente), ki so vnaprej pripravljene ali pa jih načrtamo, ko imamo določene njihove naloge
- (pod)bloke modeliramo in preizkušamo s simulacijo
- top-down je uporaben postopek za realne sisteme
 - zahteva znanje in izkušnje
- bottom-up: iz gradnikov sestavljamo vezje ali sistem
 - običajno v procesu učenja

Načrtovanje od zgoraj navzdol

POTEK

1. specifikacija
sistem




2. arhitektura
algoritem



3. implementacija
RTL, logika

RAZDELITEV

 


METODE

model sistema
(programski, matematični)

registrske operacije, FSM
podatkovna pot in krmilnik
strojno-opisna koda (HDL)
sintetizirana vezja (HLS, AI)

logika, števc, registri

Primer: digitalni sintetizator

 

Vezja s števci


- števec po modulu je lahko delilnik frekvence

Primer: števec po modulu 250 šteje od 0 do 249, ob prelivu števca negiramo signal na izhodu flip-flopa, ki ima 500x nižjo frekvenco (50 MHz $\rightarrow$ 100 kHz)

```
if div=249 then
    div <= 0
    clk1 <= not clk1
else
    div <= div + 1
end
```

- pri sinhronih vezjih (ena sama ura) uporabimo števec za omogočanje dogodkov z nižjo frekvenco
 
```
if div=9 then
    div <= 0
else
    div <= div + 1
end
en = 1 when div=0 else 0
```



Načrtovanje VHDL z umetno inteligenco (AI)

- podamo čim bolj natančno zahtevo

> Design VHDL model of a modulo 10 counter with clock input and overflow output.

✓ Specifications

- Clock input: `clk`
- Synchronous counting
- Counts 0 to 9 → wraps to 0
- Overflow output: `overflow` goes high only when counter wraps from 9 to 0
- No reset

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Modulo10_Counter is
    Port (
        clk      : in  STD_LOGIC;
        count     : out STD_LOGIC_VECTOR(3 downto 0);
        overflow  : out STD_LOGIC
    );
end Modulo10_Counter;
```

```
architecture Behavioral of Modulo10_Counter is
    signal cnt      : unsigned(3 downto 0) := (others => '0');
    signal oflow_reg : STD_LOGIC := '0';
begin

    process(clk)
    begin
        if rising_edge(clk) then
            if cnt = 9 then
                cnt      <= (others => '0');
                oflow_reg <= '1';
            else
                cnt      <= cnt + 1;
                oflow_reg <= '0';
            end if;
        end if;
    end process;

    count  <= std_logic_vector(cnt);
    overflow <= oflow_reg;

end Behavioral;
```



Numerično krmiljen oscilator

- NCO: N-bitni števec, ki se povečuje za FCW
- frekvenco določa perioda obračanja števca, uporabimo najvišji(e) bit(e) števca

Primerjava delilnika in NCO

Vhod: 50 Hz, izhod: 4 Hz (razmerje 12.5)

  - delilnik: 12 => 4.16 Hz ali 13 => 3.84 Hz
- NCO: 6-bit, FCW=5 => 3.906 Hz
- 10-bit, FCW=82 => 4.004 Hz



https://en.wikipedia.org/wiki/Numerically_controlled_oscillator

Načrtovanje NCO z AI

> Design in VHDL an NCO with 8-bit sine LUT, 32 samples, and 24-bit phase counter.

How It Works:

1. A 24-bit phase accumulator adds a phase increment every clock cycle.
2. The upper 5 bits of the accumulator select the address in a 32-entry sine lookup table (LUT).
3. The LUT returns the corresponding 8-bit sine value.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity NCO is
    Port (
        clk      : in  STD_LOGIC;
        reset    : in  STD_LOGIC;
        phase_inc : in  STD_LOGIC_VECTOR(23 downto 0); -- Tuning word
        sine_out  : out STD_LOGIC_VECTOR(7 downto 0)
    );
end NCO;
```

```
architecture Behavioral of NCO is
    signal phase_acc : unsigned(23 downto 0) := (others => '0');
    signal addr      : integer range 0 to 31 := 0;

    type sine_lut_type is array (0 to 31) of STD_LOGIC_VECTOR(7 downto 0);
    constant sine_lut : sine_lut_type := (
        -- 8-bit unsigned sine values (0 to 255), centered at 128
        -- Values scaled from  $\sin(2\pi n/32) * 127 + 128$ 
        x"80", x"98", x"AF", x"C3", x"D3", x"DF", x"E7", x"EA",
        x"E7", x"DF", x"D3", x"C3", x"AF", x"98", x"80", x"67",
        x"50", x"3C", x"2C", x"20", x"18", x"15", x"18", x"20",
        x"2C", x"3C", x"50", x"67", x"80", x"98", x"AF", x"C3"
    );

begin


    process(clk, reset)
    begin
        if reset = '1' then
            phase_acc <= (others => '0');
        elsif rising_edge(clk) then
            phase_acc <= phase_acc + unsigned(phase_inc);
        end if;
    end process;

    -- Use upper 5 bits to index 32-sample LUT
    addr <= to_integer(phase_acc(23 downto 19));
    sine_out <= sine_lut(addr);


end Behavioral;
```

Digitalno-analogna pretvorba

 - NCO izhod pošljemo na paralelni D/A pretvornik, npr:



 - ker deluje FPGA na dosti višjih frekvencah, kot je frekvenca zvoka, uporabimo 1-bitni pretvornik
 - pulzno-širinsko moduliran signal (PWM) pošljemo skozi RC sito na zvočnik



Načrtovanje PWM z AI

> Design a VHDL PWM for the NCO with an 8-bit signed data and without reset input.

Key Requirements

- Input: `sine_in` – 8-bit signed (range: -128 to +127, `std_logic_vector`)
- Output: `pwm_out` – 1-bit PWM signal
- No reset input
- Uses an internal 8-bit unsigned counter (0–255) as PWM ramp
- Maps signed sine input to unsigned threshold for PWM comparison

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity PWM_Signed is
    Port (
        clk      : in  STD_LOGIC;
        sine_in   : in  STD_LOGIC_VECTOR(7 downto 0); -- signed input (-128 to +127)
        pwm_out  : out STD_LOGIC
    );
end PWM_Signed;

architecture Behavioral of PWM_Signed is
    signal counter : unsigned(7 downto 0) := (others => '0');
    signal sine_val : signed(7 downto 0);
    signal threshold : unsigned(7 downto 0);
begin

    -- Cast input to signed
    sine_val <= signed(sine_in);

    -- Map signed range (-128 to +127) to unsigned (0 to 255)
    threshold <= unsigned(sine_val + 128);

    process(clk)
    begin
        if rising_edge(clk) then
            counter <= counter + 1;
        end if;
    end process;

    -- Generate PWM signal
    pwm_out <= '1' when counter < threshold else '0';

end Behavioral;
```

Izvedba PWM v projektu [sint25](#)


- uporabimo števec za deljenje ure
- namesto +128 naredimo **xor** 128

```
-- deljenje sistemske ure 50 MHz na 100 kHz (clk1)
process(clk)
begin
  if rising_edge(clk) then
    if div = 249 then
      div <= (others=>'0');
      clk1 <= not clk1;

      -- premakni zvok v pozitivne vrednosti
      zvokn <= unsigned(zvok xor "10000000");
    else
      div <= div + 1;
    end if;
  end if;
end process;

-- generiraj PWM izhod
pwm <= '1' when div < zvokn else '0';
```



Prikazovanje slike na monitorju VGA

 

- skeniranje vrstice (horizontala)
- - - horizontalno vračanje žarka (zatemnitev)
- ... vertikalno vračanje žarka (zatemnitev)

SVGA 800 x 600 vidnih točk @72 Hz

 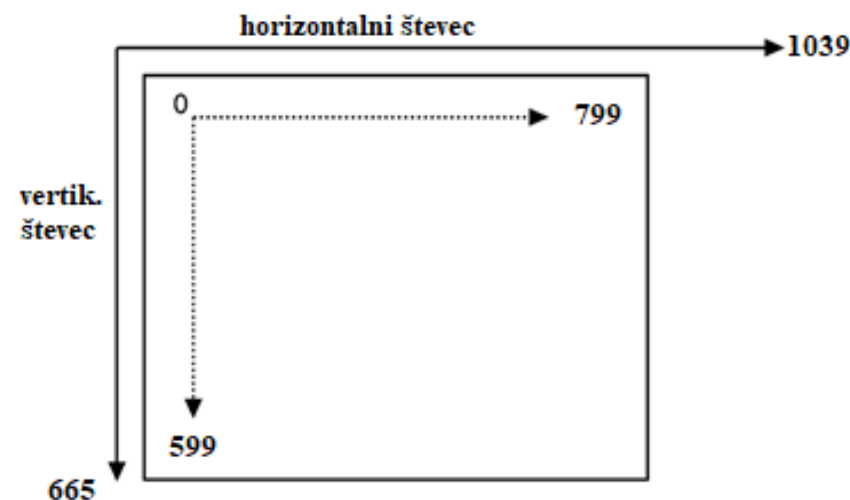- standard določa časovni potek sinhronizacije: hs, vs
- slika: $7 \cdot 10^5$ ciklov (14 ms)



VGA krmilnik

- z dvema števčema določamo koordinati trenutne točke in generiramo sinhronizacijska impulza
- časovni potek določa standard, npr. <http://tinyvga.com/vga-timing/800x600@72Hz>


```
entity vga
  x,y: out u11; -- koordinati
  hs,vs: out u1; -- sinhronizacija
begin
  if x<1039 then
    x<=x+1
  else
    x<=0
    if y<665 then
      y<=y+1
    else
      y<=0
    end
  end
end
hs = 1 when x>=856 and x<976 else 0
vs = 1 when y>=637 and y<643 else 0
end
```

ura (MHz)	horizontala (period)	start hsync	trajanje hsync	veritkala (period)	start vsync	trajanje vsync
50	1040	856	120	666	637	6


Prikaz slike iz na monitorju

- VGA priključek ima 3 analogne signale za barvo
 - na vezju so trije 2-bitni uporovni D/A pretvorniki
- dodamo logiko, ki nastavlja barvo točk (**rgb**) na določenih koordinatah v vidnem delu slike
 - kadar smo izven vidnega dela, pošljemo 0
 
```
rgb <= "000011" when (x>150 and x<550) and (y>200 and y<300) else  
      "010101" when (x<800 and y<600) else  
      "000000";
```




 $R_N = 75 \, \Omega$ $V_{CC} = 3,3 \, V$
 $V_{RGB} = 0,7 \, V$






Rotacijski inkrementalni kodirnik

 - kodirnik ima dva izhoda, ki ob vrtenju generirata impulze




Sekvenčno vezje za detekcijo vrtenja

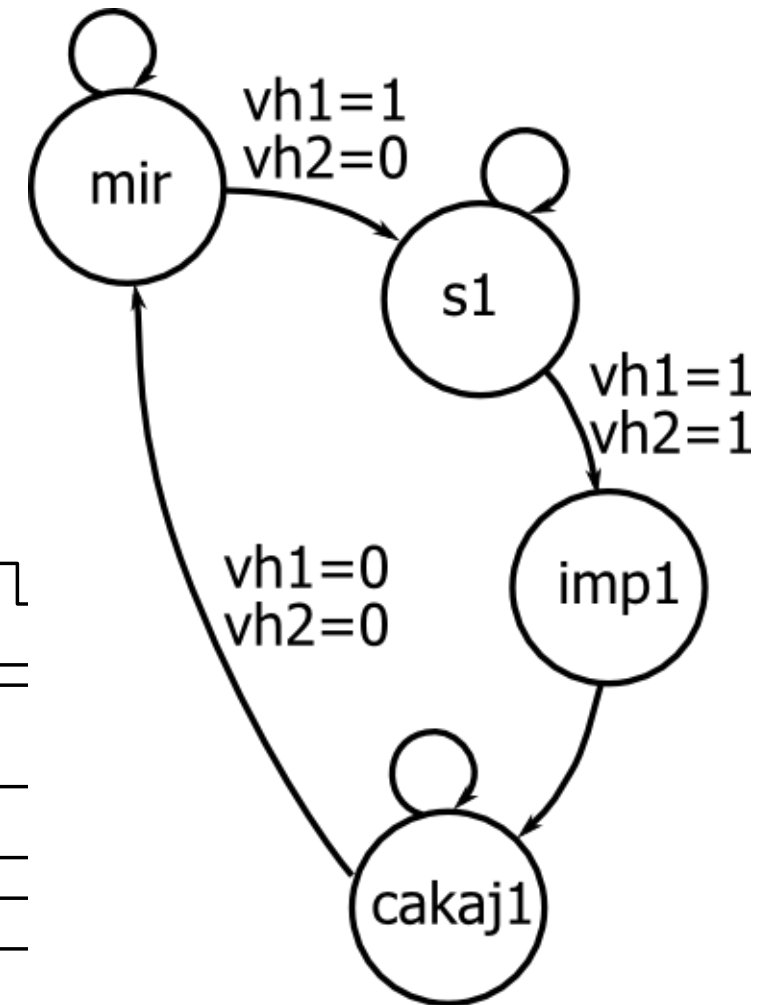  

Prototipna klaviatura


 
- 12 tipk povezanih na dva 8-bitna pomikalna registra



- Kako narediti krmilnik za branje pomikalnega registra?

Načrtovanje krmilnika

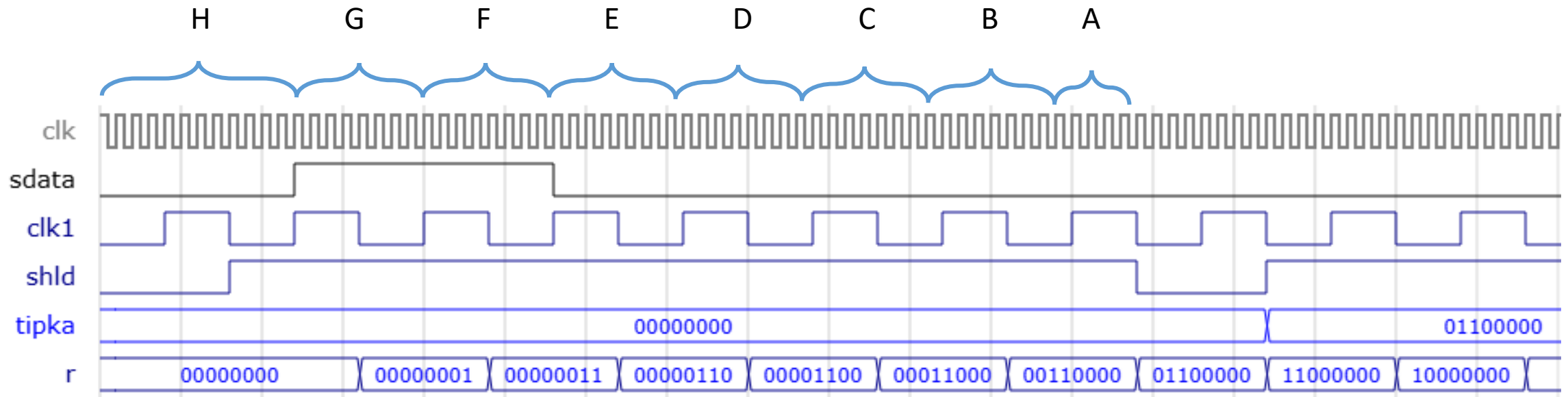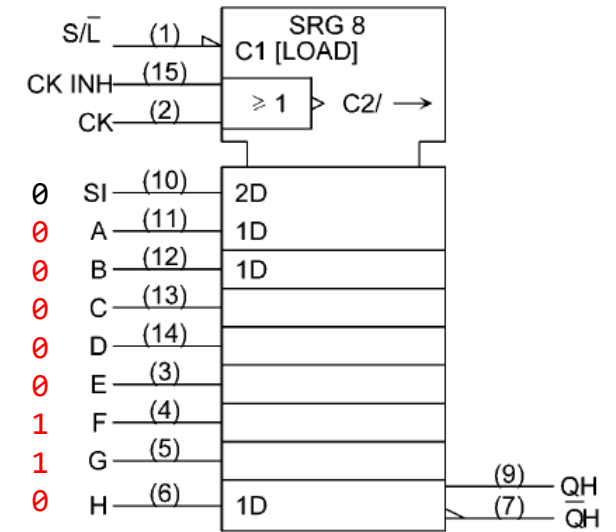- ob **shld=0** dobimo MSB (**sdata** = H)
- **shld=1** in 7x **clk1**, pomikanje bitov G-A na **sdata**
- ob padajoči fronti **clk1** pomikamo register **r**



Krmilnik v SHDL

- kako narediti krmilnik za branje dveh 74165?

```
entity vmes
  sdata: in u1;
  clk1,shld: out u1;
  tipka: out u8;
  del: u2;
  nbit: u3;
  r: u8;
begin
  del<=del+1 -- deljenje ure s 4
  if del=3 then
    clk1 <= not clk1 -- ura za 74165
    if clk1=1 then -- stoj bite in pomikaj
      nbit <= nbit + 1
      r <= r(6 downto 0) & sdata
      if shld=0 then -- prepis na izhod
        tipka <= r
      end
    end
  end
  shld = 0 when nbit=0 else 1
end
```

Krmilnik z AI

> Design VHDL model to control shift register 74165 and read serial data.

74LS165 Pin Summary (Relevant Pins):

- PL (Parallel Load): Active LOW, loads data from input pins.
- CP (Clock): Shifts bits on rising edge.
- CE (Clock Enable): Active LOW.
- QH: Serial output (connected to FPGA/microcontroller).
- D0-D7: Parallel data inputs.

VHDL Overview:

The VHDL code will:

1. Load data using the **PL** signal.
2. Pulse the **CP** signal 8 times (or however many bits you want to read).
3. Sample the **QH** pin on each clock cycle.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;


entity shift_74165_ctrl is
    Port (
        clk      : in  STD_LOGIC;
        start     : in  STD_LOGIC;
        QH_in     : in  STD_LOGIC;
        PL        : out STD_LOGIC;
        CP        : out STD_LOGIC;
        CE        : out STD_LOGIC;
        data_out  : out STD_LOGIC_VECTOR(7 downto 0);
        done      : out STD_LOGIC
    );
end shift_74165_ctrl;

architecture Behavioral of shift_74165_ctrl is
    type state_type is (IDLE, LOAD, SHIFT, DONE);
    signal state      : state_type := IDLE;
    signal bit_count  : integer range 0 to 8 := 0;
    signal shift_reg  : STD_LOGIC_VECTOR(7 downto 0) := (others => '0');
    signal cp_pulse   : STD_LOGIC := '0';
begin
    when LOAD =>
        PL    <= '0'; -- load parallel data
        CE    <= '1'; -- keep clock disabled
        CP    <= '0';
        bit_count <= 0;
        state <= SHIFT;


    when SHIFT =>
        PL    <= '1'; -- PL inactive
        CE    <= '0'; -- enable clock
        -- create one pulse on CP per cycle
        if cp_pulse = '0' then
            CP    <= '1';
            cp_pulse <= '1';
        else
            CP    <= '0';
            cp_pulse <= '0';
            shift_reg <= shift_reg(6 downto 0) & QH_in;
            bit_count <= bit_count + 1;
            if bit_count = 7 then
                state <= DONE;
            end if;
        end if;

    when DONE =>
        CE    <= '1'; -- disable clock
        CP    <= '0';
        data_out <= shift_reg;
```


- ▶ stroj končnih stanj (FSM)

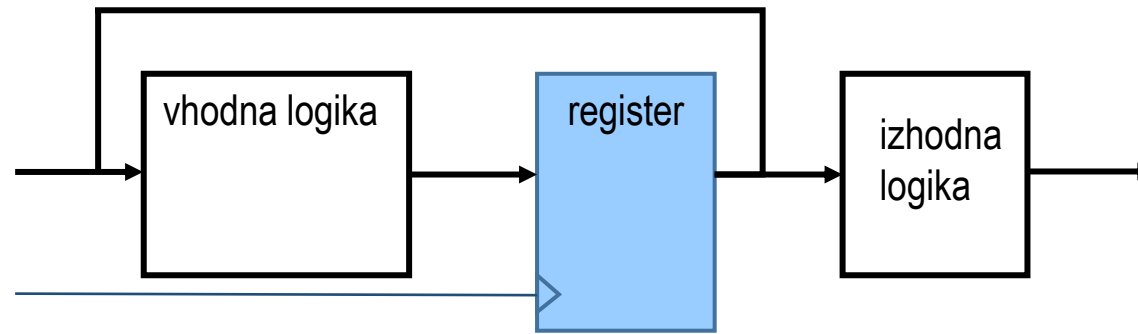

- ▶ (mikro)programiran stroj

 

Mikrosekvenčník

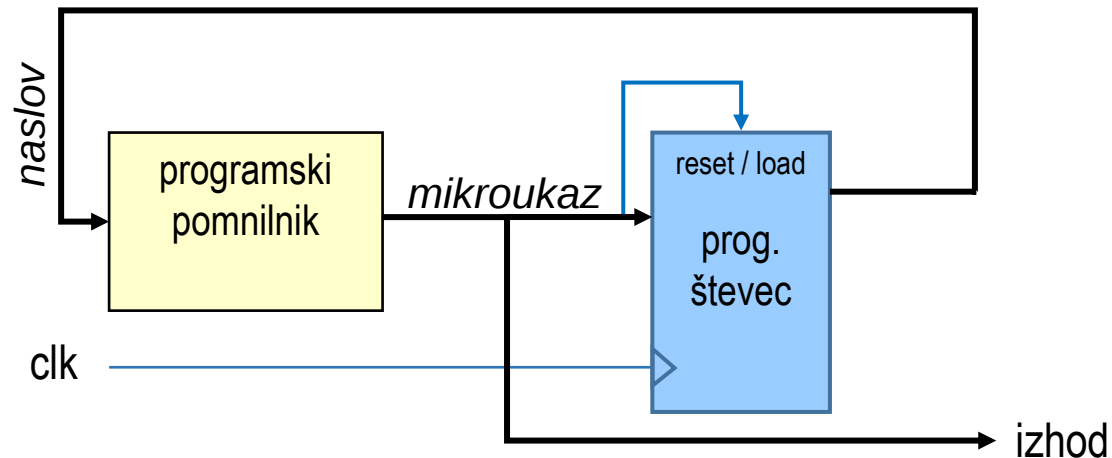

Programski števec določa zaporedje

- reset za skok na začetek
- load za skok na poljubno mesto (vejitev)

Npr. izhod: 100, 110, 001, 001, 010

- ▶ najvišji bit mikroukaza je reset

naslov	mikroukaz
000	0 100
001	0 110
010	0 001
011	0 001
100	1 010
101	x xxx
111	x xxx

Generator zaporedja z mikrosekvenčnikom

- Npr. ob start oddaj Morsejevo kodo — ...

```
entity morseB
  start: in u1;
  izh: out u1;
  en: u1
  rom: 16u2=1,1,1,0,1,0,1,0,1,2;
  data: u2;
  n: u4
begin
  data=rom(n) -- branje iz ROM
  izh=data(0) -- LSB je izhod

  if start=1 then -- start in stop
    en<=1; n<=0
  elsif data(1) then
    en<=0
  end
  if en then -- naslov pomnilnika
    n<=n+1
  end
end
```

