 


DIVS 2015, 1. vaja - povzetek

Digitalna integrirana vezja in sistemi

Kvadrirnik – VHDL koda


- ▶ pretvorba podatkovnih tipov




```
use IEEE.NUMERIC_STD.ALL;
```

```
a2 <= unsigned(a(7 downto 0)) * unsigned(a(7 downto 0));
```

Periferni vmesnik

 

 - ▶ 4 registri, ki jih pišemo in beremo preko AXI Lite



Vključitev vmesnika v kvadrirnik


► deklaracija komponente

```
architecture arch_imp of kvadrat is
  component parvmes_v1_0_S0_AXI is
    generic ( C_S_AXI_DATA_WIDTH : integer := 32;
              C_S_AXI_ADDR_WIDTH : integer := 4 );
    port ( ... );
  end component;
begin
```


► povezava komponente

```
parvmes_inst : parvmes_v1_0_S0_AXI
  port map (p0_dataout => a,
            S_AXI_ACLK => s0_axi_aclk,
            ... );
```


priključki
komponente

 


zunanji priključki
ali notranji signali

 

Simulacija s testno strukturo

 


Proceduri za pisanje in branje AXI

 

VHDL:
 
```
write32(0, 2); -- p0_dataout
write32(4, 4); -- p1_dataout
read32(8); -- a2_b2
read32(12); -- a2*b2
```



RDATA ob RVALID

Nadalnje delo

- ▶ Dopolni testno strukturo (stim_proc) z več testnimi vektorji
 - ▶ preizkus delovanja kvadrirnika pri mejnih vrednostih
- ▶ Sprememba algoritma in ali vmesnika
- ▶ Kako izdelamo nov/drugačen periferni vmesnik ?
 1. Tools > Create and Package new IP
 2. Create a new AXI 4 Peripheral
 3. nastavi lastnosti :
 4. Edit IP
 5. popravi / dopolni kodo in dodaj priključke
 6. preveri sintakso (sinteza)
 7. Review and Package IP

