



Laboratorij za načrtovanje integriranih vezij

Univerza *v Ljubljani*
Fakulteta *za elektrotehniko*




Digitalni Elektronski Sistemi

Osnove jezika VHDL

Povzetek

Entiteta (entity)

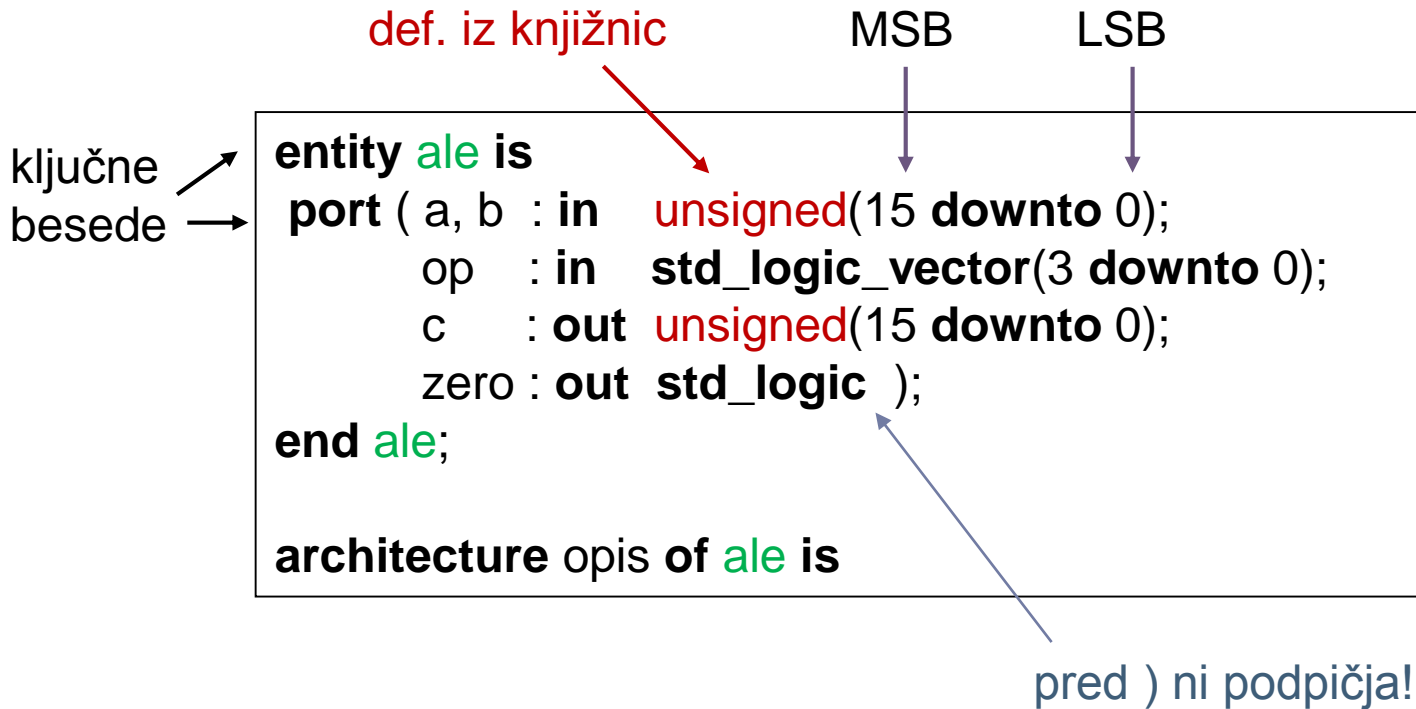- ▶ Določi **ime** vezja, parametre in priključke
 - ▶ **ime** je identifikator iz znakov: a-z, A-Z, 0-9 in _
 - ▶ prvi znak je črka, zadnji ne sme biti podčrtaj, brez čšž in presledkov



Knjižnice

- ▶ na vrhu opisa vključimo IEEE standardne knjižnice za večvrednostno logiko in numerične operacije

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.numeric_std.all;
```

- ▶ ne uporabljamo opuščениh (**deprecated**) knjižnic!

What are deprecated IEEE libraries?

Don't use `ieee.std_logic_unsigned` and similar libraries because they are not standardized. Instead, **use** `ieee.numeric_std.all`.

What's the difference between `IEEE.STD_LOGIC_ARITH.ALL` and `IEEE.NUMERIC_STD.ALL`?

`std_logic_arith` is a non-standard package created by Synopsys back in the late '80s because at the time there was no standard way to do math on signals which were not declared as integer or natural. It was "put" into the IEEE library, even though it's not an IEEE standard.

That library has now been rightly deprecated in favor of **numeric_std**.

Notranji signali in konstante

- ▶ deklaracije signalov
 - ▶ začetne vrednosti določimo z :=

```
architecture one of test is
```

```
signal count: unsigned(3 downto 0) := "0000";
```

```
signal i : integer := 0;
```

```
signal data : signed(31 downto 0) := (others=>'0');
```

```
constant zero: std_logic := '0';
```

```
constant c1: signed(9 downto 0) := to_signed(150, 10);
```

```
begin
```

vse bite na '0'



pretvorba integer v signed



Operacije z logičnimi in numeričnimi signali

▶ logične operacije

- ▶ and, or, not, nand, nor, xor

```
sum <= a xor b;
```

▶ vektorske operacije

- ▶ and, or, not, nand, nor, xor
- ▶ sestavljanje: a & b
- ▶ podvektor: a(3 **downto** 0)
- ▶ pomik: **shift_right**(a, 1)
- ▶ razteg: **resize**(a, 10)

def. iz knjižnic za
signed / unsigned

▶ aritmetične operacije

- ▶ numerični signali
- ▶ +, -, *

```
sum <= a + b;  
inc <= a + 1;  
m <= d * e;
```

podatkovni tip signed ali unsigned
ujema se po velikosti (št. bitov)

▶ velikost rezultata je:

- +,- velikost večjega operanda
- * vsota velikosti operandov

Kombinacijska logika

▶ pogojna prireditve

```
en <= bin - 30 when bin>20 else  
  bin - 20 when bin>19 else  
  bin - 10 when bin>9 else  
  bin;
```

▶ kombinacijski proces


- ▶ v oklepaju vsi signali, od katerih so odvisni izhodi procesa

```
bin2bcd: process(bin, en, de)  
begin  
  if bin>9 then  
    en <= bin - 10;  
    de <= '1';  
  else  
    en <= bin;  
    de <= '0';  
  end if;  
  bcd <= en & de;  
end process;
```

- ▶ izhod **priredimo** pri vseh komb. na vhodu (končni **else**)!

Sekvenčni gradniki

- ▶ proces s pogojem za fronto ure (**rising_edge**)
 - ▶ v oklepaju le signal ure



```
bcdstev: process (clk)
begin
  if rising_edge(clk) then
    if rst='1' then
      q <= (others=>'0');
    elsif q < 9 then
      q <= q + 1;
    else
      q <= "0000";
    end if;
  end if;
end process;
```

Opis vezja s komponentami

- ▶ deklaracija komponente in vključitev (povezava) komponent
 - ▶ component
 - ▶ port map (signal komp. => signal vezja)

architecture struktura of vezje is

component reg is

```
port ( d : in std_logic_vector(7 downto 0);  
      clk, ce : in std_logic;  
      q : out std_logic_vector(7 downto 0) );
```

end component;

```
signal en1, en2: std_logic;
```


begin

```
r1: reg port map (d=>data, clk=>clk, ce=>en1, q=>data_reg);
```

```
r2: reg port map (d=>data, clk=>clk, ce=>en2, q=>op_reg);
```

...

end struktura;

 

notranji signali

deklarirani priključki ali notranji signali vezja