





$$U_{in} = U_{ASn}$$

$$U_{out} = U_{DSn}$$

$$U_{in} = U_{DD} + U_{ASp}$$

$$U_{out} = U_{DD} + U_{DSP}$$


$$I_{Dm} = -I_{Dp}$$

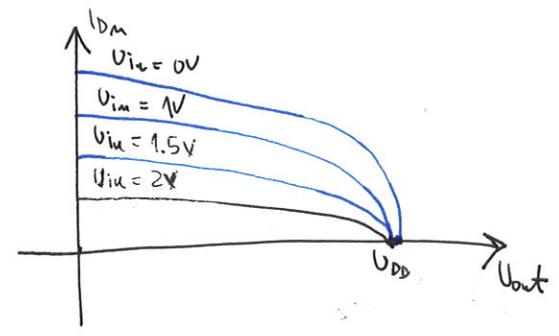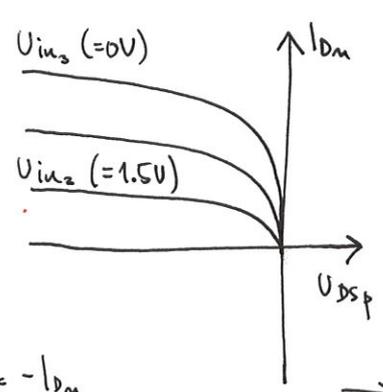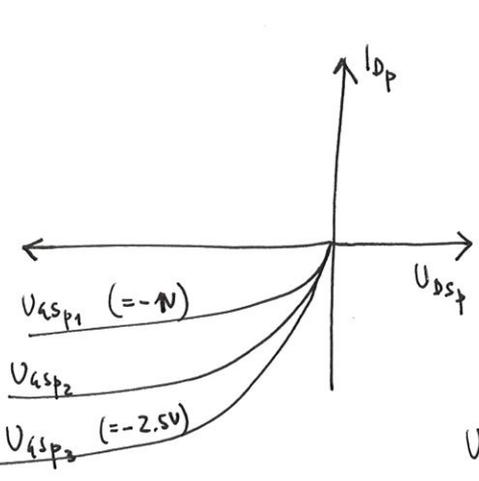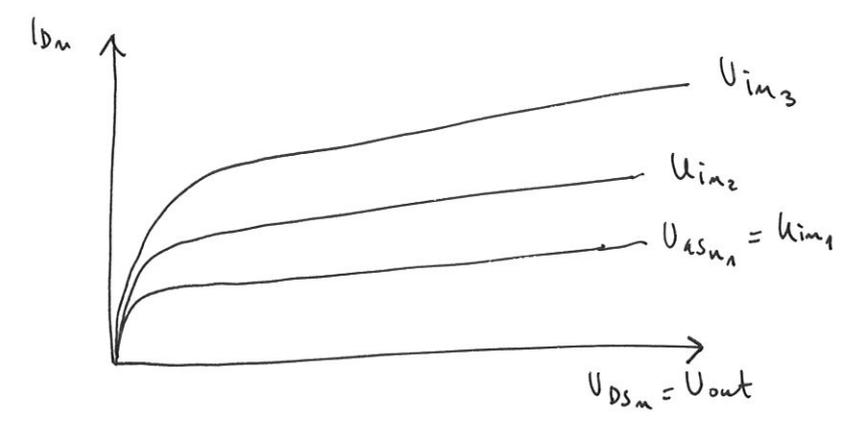


$$I_{Dp} = -I_{Dm}$$

$$U_{in} = U_{DD} + U_{ASp}$$
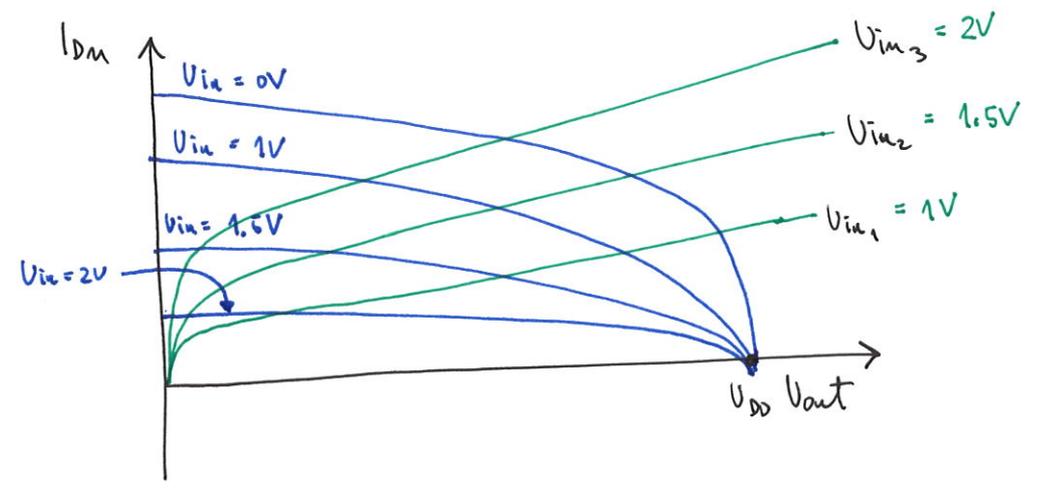
$$\Rightarrow U_{out} = U_{DD} + U_{DSP}$$



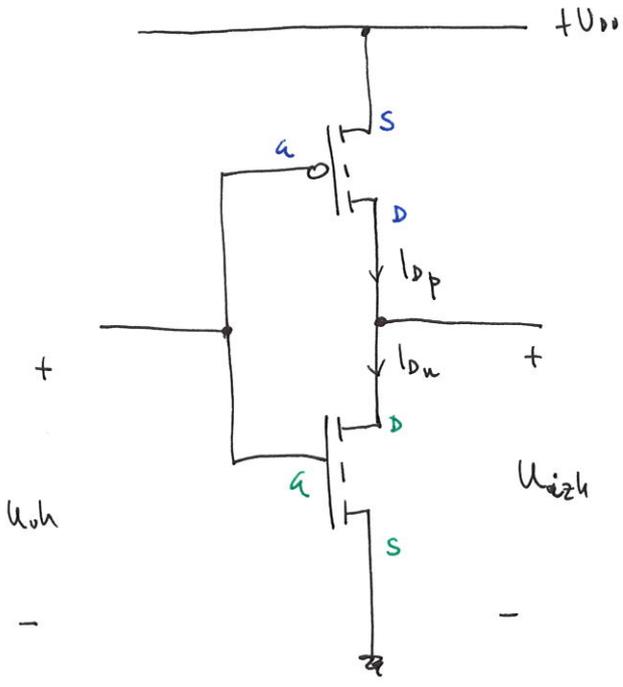

$$i_{dp} = K_p \cdot (U_{sap} - |U_{Tp}|)^2 = i_{dn} = K_n \cdot (U_{asm} - U_{Tn})^2$$

$$U_{asm} = U_{ah}$$

$$U_{sap} = U_{DD} - U_{ah}$$

$$K_p \cdot (U_{DD} - U_{ah} - |U_{Tp}|)^2 = K_n \cdot (U_{ah} - U_{Tn})^2$$

$$\sqrt{\frac{K_p}{K_n}} \cdot (U_{DD} - U_{ah} - |U_{Tp}|) = U_{ah} - U_{Tn}$$

$$\sqrt{\frac{K_p}{K_n}} \cdot (U_{DD} - |U_{Tp}|) + U_{Tn} = U_{ah} \left(1 + \sqrt{\frac{K_p}{K_n}} \right)$$

$$U_{ah} = \frac{\sqrt{\frac{K_p}{K_n}} \cdot (U_{DD} - |U_{Tp}|) + U_{Tn}}{1 + \sqrt{\frac{K_p}{K_n}}} = \frac{U_{DD}}{2}$$

1.) $\sqrt{\frac{K_p}{K_n}} = 1$
 $K_p = K_n$


$$\frac{\mu_p \cdot C_{ox}}{2} \cdot \frac{W_p}{L_p} = \frac{\mu_n \cdot C_{ox}}{2} \cdot \frac{W_n}{L_n}$$

2.)
$$U_{ah} = \frac{U_{DD} - |U_{Tp}| + U_{Tn}}{2} = \frac{U_{DD}}{2}$$

$$U_{Tn} = |U_{Tp}| ; (U_{Tp} = -U_{Tn})$$

$$\mu_p W_p = \mu_n W_n$$

$$W_p = \frac{\mu_n}{\mu_p} \cdot W_n$$

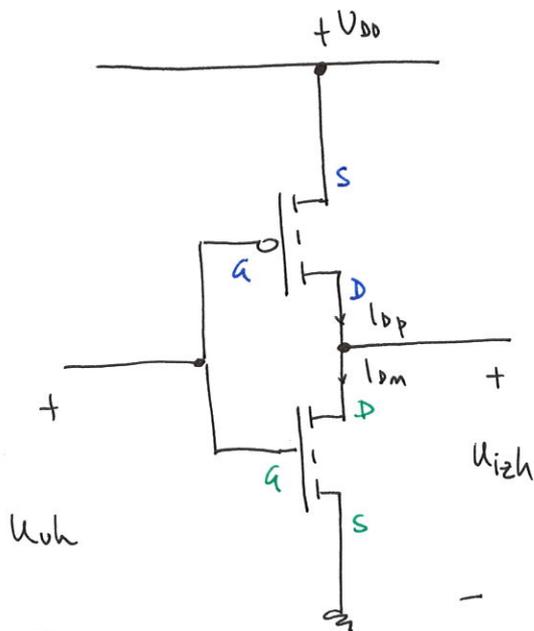


$$U_{GS_n} = u_{vh}$$

$$U_{DS_n} = u_{izh}$$

$$U_{GS_p} = u_{vh} - U_{DD}$$

$$U_{DS_p} = u_{izh} - U_{DD}$$

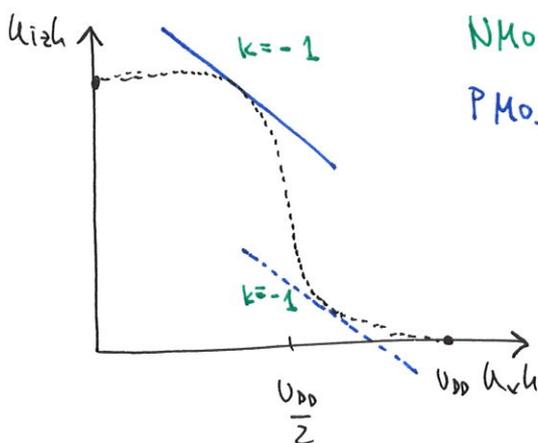

NMOS: mesičanje
PMOS: linearno podr.

$$i_{Dn} = i_{Dp}$$

$$K_n \cdot (U_{GS_n} - U_{Tn})^2 = K_p \left[2(U_{GS_p} - U_{Tp}) \cdot U_{DS_p} - U_{DS_p}^2 \right]$$

$$K_n \cdot (u_{vh} - U_{Tn})^2 = K_p \left[2 \cdot (u_{vh} - U_{DD} - U_{Tp}) \cdot (u_{izh} - U_{DD}) - (u_{izh} - U_{DD})^2 \right]$$

$$\frac{K_n}{K_p} = \beta ; \quad \beta (u_{vh} - U_{Tn})^2 = 2 \cdot (u_{vh} - U_{DD} - U_{Tp}) \cdot (u_{izh} - U_{DD}) - (u_{izh} - U_{DD})^2$$

upostevamo $\beta = 1$, $U_{Tp} = -U_{Tn}$ - in prevedimo po u_{izh}
 $U_{Tn} = U_T$

$$u_{izh}^2 - 2(u_{vh} + U_T)u_{izh} + (u_{vh} - U_T)^2 + 2(u_{vh} + U_T)U_{DD} - U_{DD}^2 = 0$$

implicitno odvajamo u_{izh} po u_{vh} in upoštevamo $\frac{du_{izh}}{du_{vh}} = -1$

$$u_{izh} = f(u_{vh})$$

odvod $u_{izh}^2 \Rightarrow 2 \cdot u_{izh} \cdot \frac{du_{izh}}{du_{vh}} = -2 \cdot u_{izh}$

$$-2 u_{izh} - 2 \left[u_{izh} - (u_{vh} + U_T) \right] + 2(u_{vh} - U_T) + 2 \cdot U_{DD} = 0$$

$$4 u_{izh} = 2(u_{vh} + U_T) + 2(u_{vh} - U_T) + 2U_{DD}$$

$$u_{izh} = u_{vh} + \frac{U_{DD}}{2}$$

mejni izhodnišni smetbo

$$u_{izh}^2 - 2(u_{vh} + U_T) \cdot u_{izh} + (u_{vh} - U_T)^2 + 2(u_{vh} + U_T) \cdot U_{DD} - U_{DD}^2 = 0$$

$$\left(u_{vh} + \frac{U_{DD}}{2}\right)^2 - 2(u_{vh} + U_T) \left(u_{vh} + \frac{U_{DD}}{2}\right) + (u_{vh} - U_T)^2 + 2(u_{vh} + U_T) \cdot U_{DD} - U_{DD}^2 = 0$$


$$u_{vh} = \frac{\frac{3}{4} \cdot U_{DD}^2 - U_T^2 - U_{DD} \cdot U_T}{2 \cdot U_{DD} - 4U_T}$$


PRIMER
 $U_{DD} = 5V$
 $U_T = 1V$

$$u_{vh} = \frac{\frac{3}{4} \cdot 25V^2 - 1V^2 - 5V \cdot 1V}{2 \cdot 5V - 4 \cdot 1V} = 2.125V$$

$$u_{izh} = u_{vh} + \frac{U_{DD}}{2} = 2.125V + 2.5V = 4.625V$$
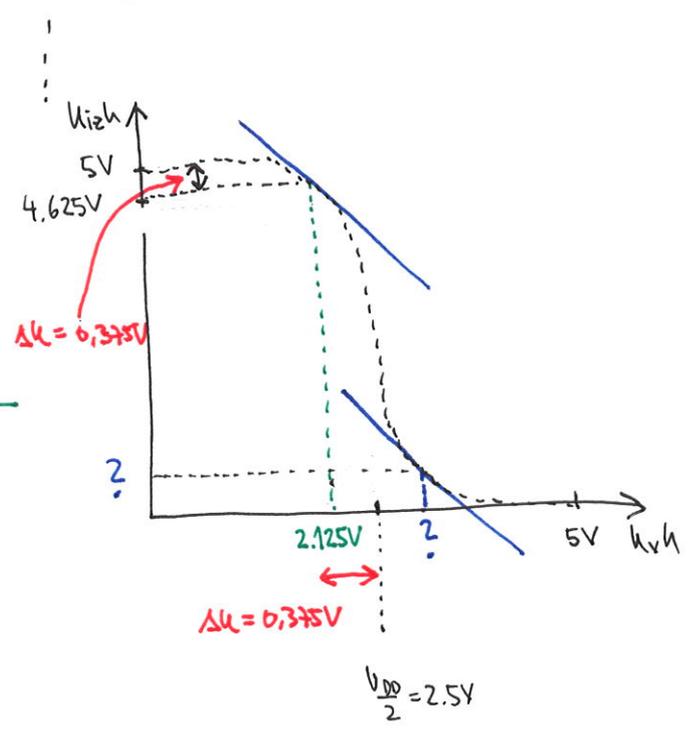
$$\Delta u_{izh} = 5V - 4.625V = 0.375V$$



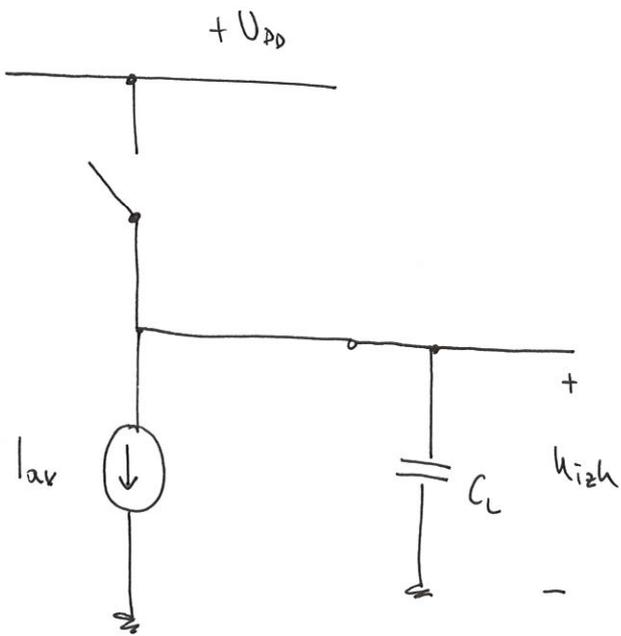

$$I_{av} = \frac{\Delta Q_{CL}}{\Delta t}$$

$$t_{pHL} \Rightarrow U_{CL}: U_{DD} \rightarrow \frac{U_{DD}}{2}$$


$$I_{av} = \frac{C_L \cdot \Delta U_{CL}}{\Delta t} \Rightarrow I_{av} = C_L \frac{\frac{U_{DD}}{2}}{t_{pHL}}$$

$$t_{pHL} = \frac{C_L \frac{U_{DD}}{2}}{I_{av}}$$

$$U_{DD} = U_{SWING}$$


$$U_{SWING} = U_{act}^{("1")} - U_{act}^{("0")}$$
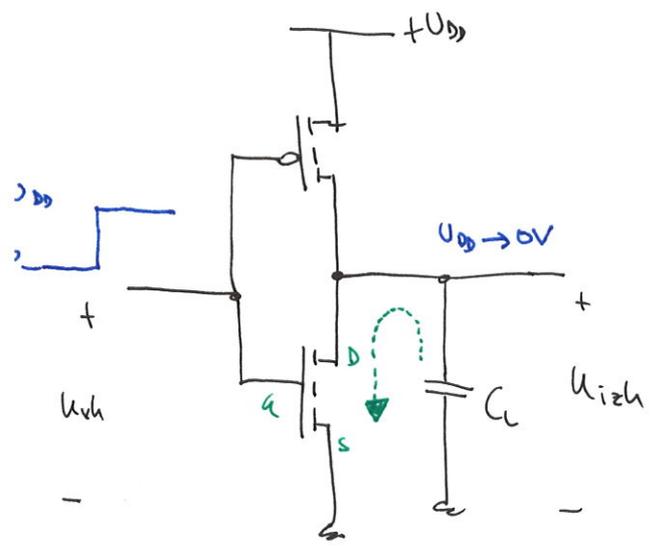
$$t_{pHL} = \sim \frac{C_L \cdot U_{DD}}{I_{av}}$$




$$u_{vk} = U_{GSm}$$

$$u_{kzh} = U_{DSm} = u_{Ck}$$

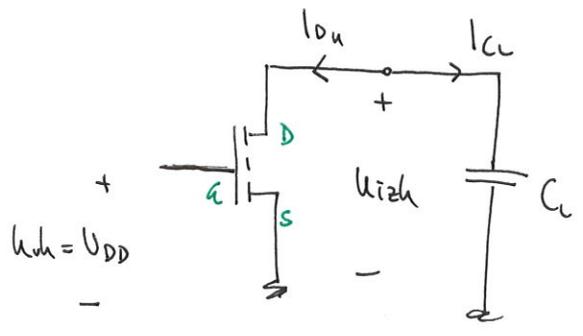
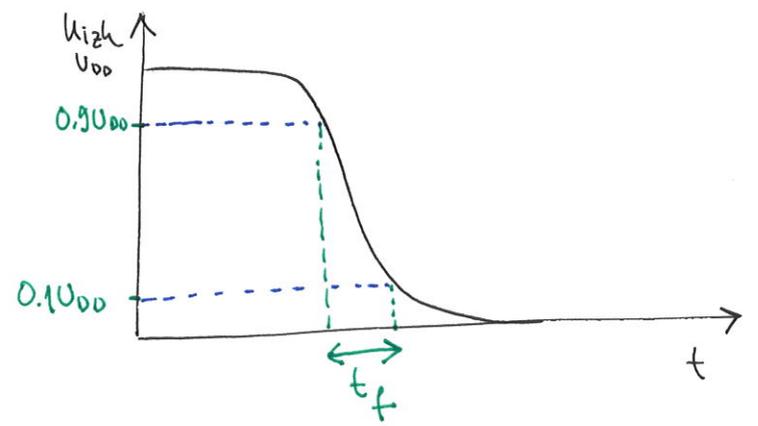
$$I_{Ck} = C \frac{du_{Ck}}{dt} = C \frac{du_{kzh}}{dt}$$



$$0.1 U_{DD} \leq u_{kzh} \leq 0.9 U_{DD}$$

$$t_f = t_{f1} + t_{f2}$$

1.) t_{f1} : UKOS N NABEĆENJU

$$U_{DD} - U_{Tn} \leq u_{kzh} \leq 0.9 U_{DD}$$

2.) t_{f2} UKOS N LIN. PODROĆU

$$0.1 U_{DD} \leq u_{kzh} \leq U_{DD} - U_{Tn}$$



MEJA MED NABEĆENJEM I LIN. PODROĆEM

$$U_{DS} = U_{GS} - U_{Tn}$$

$$\uparrow$$

$$U_{DD}$$

$$U_{DS} = U_{DD} - U_{Tn}$$

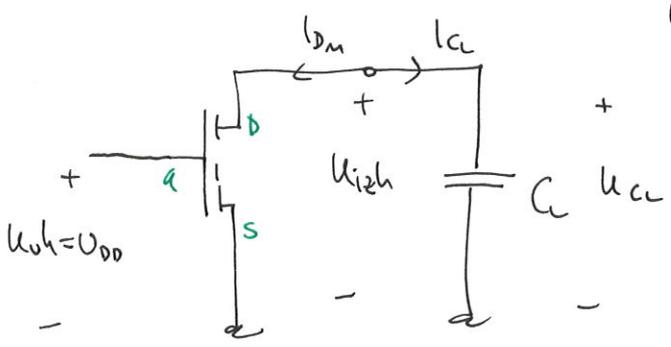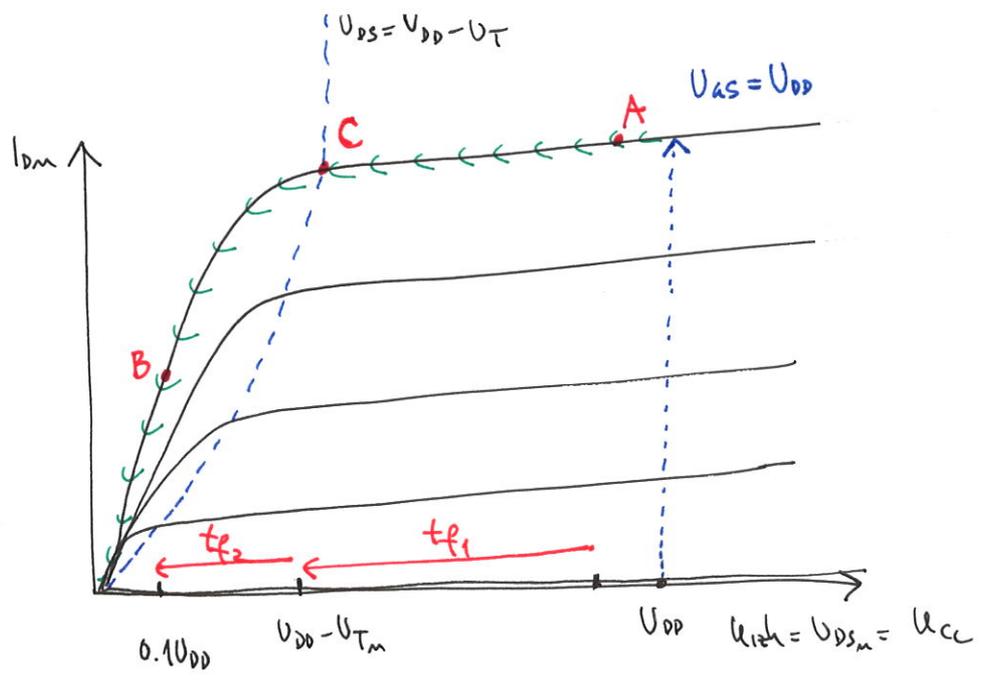

1.) NASTIČENJE, t_{f1}

$$I_{CL} = -I_{DM}$$

$$I_{CL} + I_{DM} = 0$$

$$C_L \frac{dU_{CC}}{dt} + K_M \cdot (U_{DS,sat} - U_{TM})^2 = 0$$

$$C_L \frac{dU_{DS}}{dt} + K_M (U_{DD} - U_{TM})^2 = 0$$

$$dU_{DS} = - \frac{K_M}{C_L} (U_{DD} - U_{TM})^2 dt$$

$$\int_{U_{DD} - U_{TM}}^{0.9U_{DD}} dU_{DS} = - \frac{K_M}{C_L} \cdot (U_{DD} - U_{TM})^2 \cdot \int_0^{t_{f1}} dt$$

$$U_{DD} - U_{TM} - 0.9U_{DD} = - \frac{K_M}{C_L} \cdot (U_{DD} - U_{TM})^2 \cdot t_{f1}$$

$$0.1U_{DD} - U_{TM}$$

$$U_{TM} - 0.1U_{DD} = - \frac{K_M}{C_L} (U_{DD} - U_{TM})^2 \cdot t_{f1}$$

$$t_{f1} = \frac{(U_{TM} - 0.1U_{DD}) \cdot C_L}{K_M \cdot (U_{DD} - U_{TM})^2}$$

PRIMER: $U_{TM} = 0.2 U_{DD}$

$$t_{f1} = \frac{1}{10} \cdot U_{DD} \cdot C_L \cdot \frac{1}{K_M \cdot \frac{16}{25} \cdot U_{DD}^2} = \frac{5}{32} \cdot \frac{C_L}{K_M \cdot U_{DD}}$$

2. L.W. PODROČJE, t_{p2}

8

$$C_L \frac{d u_{ce}}{dt} + K_N \cdot \left[2 \cdot (U_{GS_n} - U_{T_n}) U_{DS_m} - U_{DS_m}^2 \right] = 0$$

$$C_L \frac{d u_{izh}}{dt} + K_N \cdot \left[2 \cdot (U_{DD} - U_{T_n}) u_{izh} - u_{izh}^2 \right] = 0$$

$$C_L \frac{d u_{izh}}{K_N \cdot \left[2 \cdot (U_{DD} - U_{T_n}) u_{izh} - u_{izh}^2 \right]} = -dt$$

$$\frac{C_L}{K_N \cdot 2 \cdot (U_{DD} - U_{T_n})} \int_{U_{DD} - U_{T_n}}^{0 \cdot U_{DD}} \frac{d u_{izh}}{\frac{u_{izh}^2}{2(U_{DD} - U_{T_n})} - u_{izh}} = \int dt$$

$$\int \frac{d u_{izh}}{\frac{u_{izh}^2}{2(U_{DD} - U_{T_n})} - u_{izh}} \Rightarrow \int \frac{dx}{C x^2 - x} \Rightarrow \frac{1}{x(Cx - 1)} = \frac{A}{x} + \frac{B}{Cx - 1}$$

$$C = \frac{1}{2(U_{DD} - U_{T_n})}$$

$$1 = A \cdot Cx - A + Bx$$

$$A = -1$$

$$0 = AC + B$$

$$\int \frac{d u_{izh}}{C \cdot u_{izh}^2 - u_{izh}} = \int \frac{(-1)}{u_{izh}} \cdot d u_{izh} + \int \frac{C}{C \cdot u_{izh} - 1} \cdot d u_{izh} \quad 0 = -C + B \Rightarrow B = C$$

$$= - \int \frac{d u_{izh}}{u_{izh}} + \int \frac{\frac{1}{2(U_{DD} - U_{T_n})}}{\frac{u_{izh}}{2(U_{DD} - U_{T_n})} - 1} \cdot d u_{izh}$$

$$= \frac{C_L}{K_p \cdot 2(V_{DD} - V_{Th})} \cdot \left[(-1) \cdot \int_{V_{DD} - V_{Th}}^{0.1V_{DD}} \frac{dv_{izh}}{v_{izh}} + \int_{V_{DD} - V_{Th}}^{0.1V_{DD}} \frac{dv_{izh}}{v_{izh} - 2(V_{DD} - V_{Th})} \right]$$

$$= \frac{C_L}{2K_p \cdot (V_{DD} - V_{Th})} \left[\ln \frac{V_{DD} - V_{Th}}{0.1V_{DD}} + \ln \frac{0.1V_{DD} - 2(V_{DD} - V_{Th})}{V_{DD} - V_{Th} - 2(V_{DD} - V_{Th})} \right]$$

PRIMER $V_{Th} = 0.2V_{DD}$

$$= \frac{C_L}{2 \cdot K_p \cdot \frac{4}{5} \cdot V_{DD}} \cdot \left[\ln \frac{\frac{4}{5} \cdot V_{DD}}{\frac{1}{10} \cdot V_{DD}} + \ln \frac{\frac{1}{10} \cdot V_{DD} - 2 \cdot \frac{4}{5} \cdot V_{DD}}{-\frac{4}{5} \cdot V_{DD}} \right]$$

$$= \frac{C_L}{\frac{8}{5} \cdot K_p \cdot V_{DD}} \cdot \left[\ln 8 + \ln \frac{15}{8} \right] \quad \ln x \cdot y = \ln x + \ln y$$

$$t_{f2} = \frac{5}{8} \cdot \frac{C_L}{K_p \cdot V_{DD}} \cdot \ln 15$$

$$t_{f2} = 1.69 \frac{C_L}{K_p \cdot V_{DD}}$$

$$t_f = t_{f1} + t_{f2}$$

$$t_f = \left(\frac{5}{32} + 1.69 \right) \cdot \frac{C_L}{K_p \cdot V_{DD}}$$

$$t_f = 1.85 \cdot \frac{C_L}{K_p \cdot V_{DD}}$$