

Digital Integrated Circuits and Systems

Andrej Trost

Lab 1: Basic arithmetic operations and averaging filter

Tool: Vivado 2025.1

Task: design a circuit model for basic operations, analyze implementation, make an averaging filter, analyze the implementations and verify operation with simulation



Technology & boards

AMD (Xilinx) Zynq

- FPGA + ARM Cortex-A9

	Z-7007S	Z-7010	Z-7020
LUT (DFF)	14k (29k)	17k (35k)	53k (106k)
BRAM	200 KB	240 KB	560 KB
DSP	66	80	220
I/O	50-100	100	200

MiniZed
Cora Z7




RedPitaya



ZedBoard



Chip

 

Programmable logic for
signal processing
CPU for control tasks

Design flow

- ▼ PROJECT MANAGER
 - ⚙ Settings
 - Add Sources
 - Language Templates
- ⚙ IP Catalog
- > IP INTEGRATOR
- > SIMULATION
- > RTL ANALYSIS
- ▼ SYNTHESIS
 - ▶ Run Synthesis
 - > Open Synthesized Design
- ▼ IMPLEMENTATION
 - ▶ Run Implementation
 - > Open Implemented Design
- ▼ PROGRAM AND DEBUG
 - ⬇️ Generate Bitstream
 - > Open Hardware Manager

Vivado 2025.1

Main tasks

Active view

Status

Close

Console

Reports

The screenshot displays the Vivado 2025.1 IDE interface for a project named 'ndes1'. The interface is divided into several panes:

- Flow Navigator (Left):** Contains project management tasks such as 'Settings', 'Add Sources', 'Language Templates', 'IP Catalog', 'Create Block Design', 'Open Block Design', 'Generate Block Design', 'Run Simulation', 'Run Linter', 'Open Elaborated Design', 'Report Methodology', 'Report DRC', 'Report Noise', 'Schematic', and 'Run Synthesis'.
- Sources & Properties (Top Left):** Shows the project hierarchy with 'Design Sources (1)' (regop (regop.sv)), 'Constraints (1)' (constrs_1 (1)), and 'Simulation Sources (1)'. It also displays 'Synthesis Run Properties' for 'synth_1'.
- Schematic (Center):** Displays a circuit diagram with three registers (reg_a_reg[13:0], reg_b_reg[13:0], reg_c_reg[13:0]) and a divider (RTL_DIV). The registers are connected to a clock (clk) and data inputs (a[13:0], b[13:0]). The divider takes inputs i0[13:0] and i1[13:0] and produces output o[13:0].
- Reports (Bottom):** A table showing the status of various design runs.

The top status bar indicates 'Implementation Complete' with a green checkmark and a 'Default Layout' dropdown. The bottom status bar shows the 'Design Runs' table.

Name	Constraints	Status	WNS	TNS	WHS	THS	WBSS	TPWS	Total Power	Failed Routes	Methodology	RQA Score	LUT	QoR Suggest
✓ synth_1	constrs_1	synth_design Complete!											209	
✓ impl_1	constrs_1	route_design Complete!	62.818	0.000	0.358	0.000		0.000	0.093	0	42 Warn		209	

Model registered operations (add, multiply, divide)

1. Create Vivado project

- device: MiniZed (xc7z007sclg225-1)
- constraints: 100 MHz or 10 MHz clock

```
create_clock -name clk -period 10.000 [get_ports clk];
```

2. Design source: regop.sv (SystemVerilog)

- 14 or 28-bit operation with registers

3. Run Synthesis

- check utilization and delay (Data Path Delay)

```
Tcl: report_timing -delay_type max -max_paths 1
```

4. Run Implementation

- report timing and get precise delay info (clk period - WNS)
- record utilization and max. clock frequency

```
module regop(  
    input logic          clk,  
    input logic  [13:0] a,b,  
    output logic  [13:0] reg_c  
);  
  
    logic [13:0] reg_a, reg_b;  
    logic [13:0] c;  
  
    always_ff @(posedge clk) begin  
        reg_a <= a;  
        reg_b <= b;  
        reg_c <= c;  
    end  
  
    assign c = reg_a + reg_b;  
endmodule
```

Report

circuit	LUT / FF / DSP	Data Path Delay [ns]	Logic levels	clk period [ns]	frequency [MHz]
add 14					
add 28					
mul 14					
mul 28					
div 14					
div 28					

Design averaging filter

- compute average of last three samples
- use internal buffers
- check with provided testbench
- explore options for division (1/3)
 - division by power of 2
 - integer divider
 - approximate with multiplication, 11/32

```
module avg_filter(  
    input logic clk,  
    input logic signed [13:0] a,  
    output logic signed [13:0] avg  
);  
    logic signed [13:0] z [0:2];  
    logic signed [15:0] s;  
  
    always_ff @(posedge clk) begin  
        z[0] <= a;  
        z[1] <= z[0];  
        z[2] <= z[1];  
        avg <= ...  
    end  
  
    assign s = z[0] + z[1] ...
```

circuit	LUT / FF / DSP	Data Path Delay [ns]	Logic levels	clk period [ns]	frequency [MHz]