



Laboratorij za načrtovanje integriranih vezij

Univerza v Ljubljani  
Fakulteta za elektrotehniko



## Preizkušanje elektronskih vezij

Generacija testnih vzorcev  
Test pattern generation

# Overview

---

- ▶ Introduction
- ▶ Theoretical Background in Boolean Difference
- ▶ Designing a Stuck-at ATPG for Combinational Circuits
- ▶ Designing a Sequential ATPG
- ▶ ATPG for Non-Stuck-At Faults
- ▶ Other Issues in Test Generation

# Introduction


---

- ▶ Test generation is the task of **searching for a test pattern** that will detect a specific fault.
- ▶ This process is called **ATPG – Automatic Test Pattern Generation**.
- ▶ Without powerful and efficient ATPG, chips will mostly depend on design for testability techniques (-> increasing area and cost).
- ▶ ATPG is one of the most important, challenging and difficult problem.
- ▶ The goal of this chapter is to present ATPG techniques for various fault models.
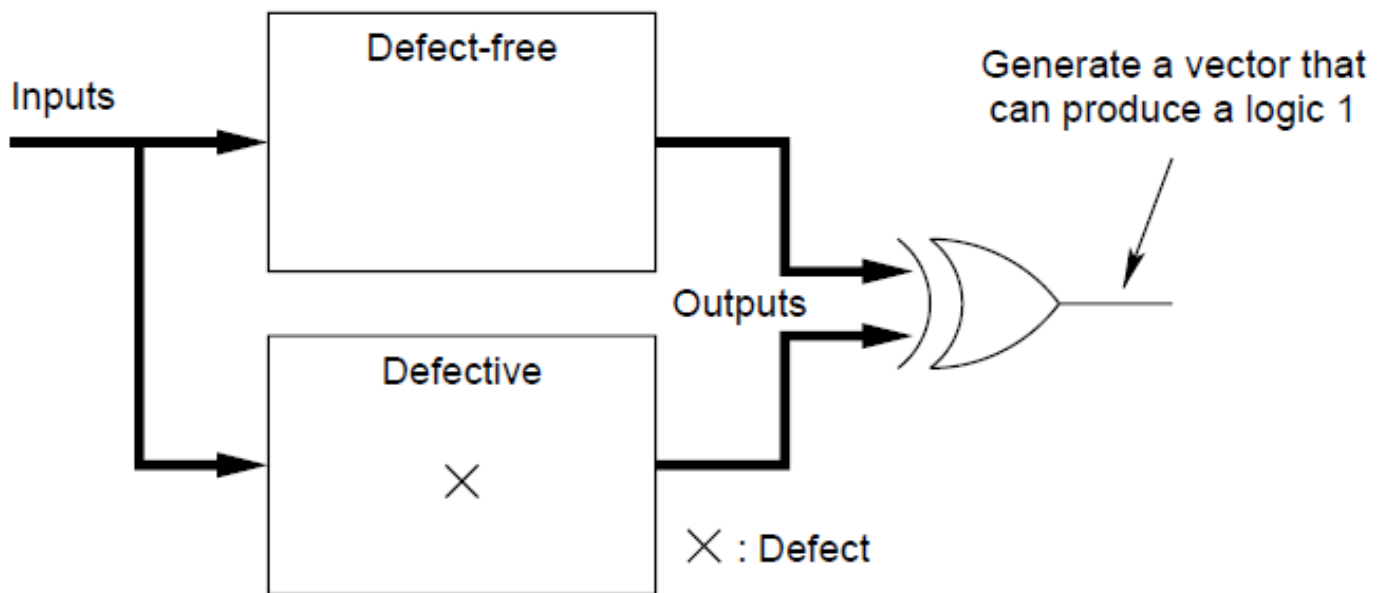
# Introduction

---

- ▶ For any defective chip, which is functionally different from the defect-free chip, there must exist at least one input (test vector) that can differentiate both chips.
- ▶ The goal of ATPG is to efficiently generate that test vector.



# Introduction


---

- ▶ If ATPG is capable to deliver high-quality test patterns (high fault coverage and small test set), DFT is no longer necessary.
- ▶ As it is difficult to generate test vectors targeting all possible, ATPG operate on an abstract representation of defects, referred as faults.
- ▶ The most popular and used fault model is single stuck-at fault model.
 
# Introduction

---

- ▶ Single stuck-at fault model assumes that a circuit node is tied to logic 1 or logic 0
  - ▶ single stuck-at 1, s-s-1
  - ▶ single stuck-at 0, s-s-0
- ▶ Consider the single stuck-at 1 at node  $d$  ( $d/1$ ).
- ▶ First, we have to activate the fault, i.e. to find the difference between the fault-free circuit and the circuit with the fault  $d/1$ .
- ▶ Then, we have to propagate information about the fault (fault signal) to the circuit output node.



# Introduction

---

- ▶ ATPG systems attempts to generate test vectors for every possible fault in the circuit.
- ▶ In this example, other faults  $d/0$ ,  $a/0$ ,  $a/1$ ,  $b/0$ , are targeted by ATPG.
- ▶ As some of the faults in the circuit can be logically equivalent, no test can be obtained to distinguish between (these faults form a set of equivalent faults).
- ▶ Therefore, fault collapsing is used before ATPG in order to reduce the number of faults to consider.

# Random Test Generation

---


- ▶ Random Test generation (RTG) is one of the simplest methods for generating vectors.
- ▶ Test vectors are randomly generated and fault simulated (fault graded) on the circuit under test (CUT).
- ▶ Because no specific fault is targeted, the RTG complexity is low.
- ▶ Disadvantages of RTG are large test set size and not sufficiently high fault coverage.
- ▶ Logic values are randomly generated at the primary inputs, with equal probability of assigning a logic 1 or logic 0 to each primary input.
- ▶ Note, that pseudo-random generator is most often used -  
> repeated test set with the same pseudo-random generator.


 
# Random Test Generation


---

- ▶ **Level of confidence** on a random test set  $T$  can be measured as the probability that  $T$  can detect all stuck-at faults in the circuit.
- ▶ For  $N$  random vectors, the test quality  $t_N$  indicates that all detectable stuck-at faults are detected by these  $N$  random vectors.
- ▶ Some faults (**random-pattern resistant faults**) are difficult to test with RTG. Example:


 
# Random Test Generation

- ▶ To target random-pattern resistant faults, biasing is required -> input vectors are no longer uniformly distributed.
- ▶ Determining the optimal bias values for each primary input is difficult task.
- ▶ Minimum detection probability of a detectable fault  $f$  can be determined by the output cone in which  $f$  resides.



# Exhaustive Test Generation


---

- ▶ If the combinationa circuit has few primary inputs, **exhaustive testing (ET)** is a viable option.
- ▶ Every possible input vector is enumerated.
- ▶ This is superior to RTG since RTG can produce duplicated vectors.
- ▶ For large circuit, ET is impractical.
- ▶ But, it may be possible to partition the circuit and only exhaust the input vectors within each cone (pseudo-exhaustive testing, **PET**).
- ▶ For the circuit with three PO, each with corresponding cone with  $n_1$ ,  $n_2$  and  $n_3$  PI, the number of PET is at most  $2^{n_1} + 2^{n_2} + 2^{n_3}$
 
# Theoretical Background: Boolean Difference

---


- ▶ Consider s-s-0 on primary input  $y$  ( $y$  s-s-0).
- ▶ Faulty circuit  $f' = f(y=0)$
- ▶ Test vector must satisfy equation:  
 $f(y=1) \text{ EX-OR } f(y=0) = 1$
- ▶ Also, fault must be first excited:
  - ▶  $y \cdot f(y=1) \text{ EX-OR } f(y=0) = 1$
  - ▶  $f(y=1) \text{ EX-OR } f(y=0)$  is called **Boolean Difference** of  $f$  with respect to  $y$


 
# Untestable Fault

---

- ▶ If there exists no input vector to test a certain fault, the fault is **untestable** (or **redundant**)
- ▶ Consider the fault  $z/0$ .



# Stuck-at ATPG for Combinational Circuits

---

- ▶ In ATPG, there are two main tasks:
  - ▶ 1) Excitation of target fault
  - ▶ 2) Propagation of the fault to the primary output
- ▶ Logic values for fault-free and faulty circuit are needed ( $v$  and  $v_f$ ).
- ▶ 5-valued algebra (Roth):  $0, 1, X, D$  and  $D'$  is used.
  - ▶  $D = 1/0$  and  $D' = 0/1$ .
- ▶ Boolean operators (AND, OR, NOT, XOR) can be used on 5-valued algebra.
- ▶ The simplest way to perform Boolean operations is to represent each component value into the  $v/v_f$  form and perform Boolean operations on fault-free and faulty value separately.

# Boolean operation for 5-valued algebra

---

AND Operation

AND	0	1	D	$\bar{D}$	X
0	0	0	0	0	0
1	0	1	D	$\bar{D}$	X
D	0	D	D	0	X
$\bar{D}$	0	$\bar{D}$	0	$\bar{D}$	X
X	0	X	X	X	X

OR Operation

OR	0	1	D	$\bar{D}$	X
0	0	1	D	$\bar{D}$	X
1	1	1	1	1	1
D	D	1	D	1	X
$\bar{D}$	$\bar{D}$	1	1	$\bar{D}$	X
X	X	1	X	X	X

NOT Operation

NOT	
0	1
1	0
D	$\bar{D}$
$\bar{D}$	D
X	X

# Naive ATPG Algorithm

---

- ▶ Worst-case computational complexity is exponential.
- ▶ All possible input patterns may have to be tried before a vector is found or that the fault is declared as undetectable.
- ▶ Intelligence mechanism can be used to reduce the search space.

---

## Algorithm 1 Naive ATPG ( $C, f$ )

---

```
1: while a fault-effect of  $f$  has not propagated to a PO and all possible vector combinations have not been tried do  
2:   pick a vector,  $v$ , that has not been tried;  
3:   fault simulate  $v$  on the circuit  $C$  with fault  $f$ ;  
4: end while
```

---



# ATPG Algorithm


---

- ▶ ATPG may make a wrong **decision** for specific logic value on PI.
- ▶ In this case, the decision should be altered (opposite logic value) on PI.
- ▶ The process of making decisions and reversing decisions results in a **decision tree**.
- ▶ Each node in the decision tree represents a decision variable.
- ▶ If only two choices are possible for each decision variable, decision tree is a **binary tree**.
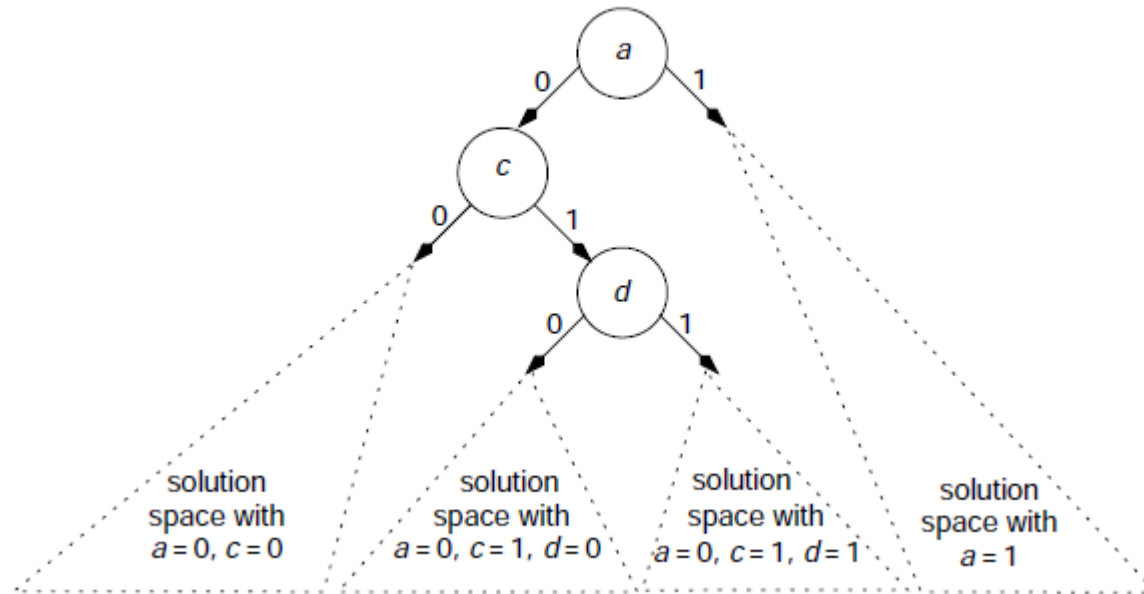
# Decision Tree

---


- ▶ Example of decision tree.
- ▶ At each decision, the search space is halved.
- ▶ If a test vector exists, there must be a path along the decision tree that leads to the test vector.


 
# Backtracking

---

- ▶ Whenever a conflict is detected, the search must return to some earlier point in decision process.
- ▶ The reversal of decision is called a **backtrack**.
- ▶ The easiest mechanism to keep track of decisions is to reverse the most recent decision made.
- ▶ When reversing any decision, the signal values implied by the assignment of the previous decision variables must be undone.



# Basic ATPG Algorithm

---

- ▶ Given a target fault  $g/v$  in a fanout-free combinational circuit  $C$ , procedure to generate a vector for the fault (Algorithm 2).
- ▶ Functions `JustifyFanoutFree()` and `PropagateFanoutFree()` are recursive functions.

---

**Algorithm 2** Basic Fanout Free ATPG ( $C, g/v$ )

---

- 1: initialize circuit by setting all values to  $X$ ;
  - 2: `JustifyFanoutFree( $C, g, \bar{v}$ )`; /\* excite the fault by justifying line  $g$  to  $\bar{v}$  \*/
  - 3: `PropagateFanoutFree( $C, g$ )`; /\* propagate fault-effect from  $g$  to a PO \*/
-

# Basic ATPG Algorithm

---

- ▶ `JustifyFanoutFree(g, v)` recursively justifies predecessor signal of  $g$  until all signals that should be justified are justified from the PI.

---

## Algorithm 3 `JustifyFanoutFree(C, g, v)`

---


```
1:  $g = v$ ;  
2: if gate type of  $g ==$  primary input then  
3:   return;  
4: else if gate type of  $g ==$  AND gate then  
5:   if  $v == 1$  then  
6:     for all inputs  $h$  of  $g$  do  
7:       JustifyFanoutFree(C, h, 1);  
8:     end for  
9:   else  $\{v == 0\}$   
10:     $h =$  pick one input of  $g$  whose value  $== X$ ;  
11:    JustifyFanoutFree(C, h, 0);  
12:  end if  
13: else if gate type of  $g ==$  OR gate then  
14:   ...  
15: end if
```

---
 
# Justify Function

---

- ▶ Example circuit  $C$ , justify  $g=1$




call #1: `JustifyFanoutFree(C, g, 1)`  
call #2: `JustifyFanoutFree(C, a, 1)`  
call #3: `JustifyFanoutFree(C, f, 1)`  
call #5: `JustifyFanoutFree(C, c, 0)`

Input vector  $abcd = 1X0X$  justifies  $g=1$

# Justify Function

---

- ▶ Example circuit C, justify  $g=1$

 


call #1: JustifyFanoutFree( $C, g, 1$ )  
call #2: JustifyFanoutFree( $C, a, 1$ )  
call #3: JustifyFanoutFree( $C, f, 1$ )  
call #4: JustifyFanoutFree( $C, d, 0$ )  
call #5: JustifyFanoutFree( $C, c, 0$ )

Input vector  $abc = 1X0$  justifies  $g=1$
 
# Justify Function

---

- ▶ In fanout-free circuit, JustifyFanoutFree() routine will always be able to set  $g$  to the desired value  $v$  and no conflict will occur.
- ▶ This is not true for circuits with fanout branches -> two or more signals tracing back to the same fanout stem are correlated.
- ▶ For example, justifying  $d=1$  is impossible (conflict on  $a$ )





 
# Justify Function

---

- ▶ Example circuit C, justify  $z=0$
- ▶ Due to fanout structure, choices for decisions are limited.



# Propagate Function

---

- ▶ Once the fault is excited, the next step is to propagate the fault-effect to PO.
- ▶ PropagateFanoutFree() is also a recursive function.
- ▶ The fault-effect is propagated one gate at a time until it reaches PO.
- ▶ Example: propagate  $D$  at  $g$  to PO  $z$ .

call #1: PropagateFanoutFree( $C$ ,  $g$ )

call #2: JustifyFanoutFree( $C$ ,  $h$ , 0)

call #3: JustifyFanoutFree( $C$ ,  $b$ , 0)

call #4: PropagateFanoutFree( $C$ ,  $z$ )

Input vector  $abc = 100$  justifies  $g=1$

# Propagate Function Algorithm

---

**Algorithm 4** PropagateFanoutFree( $C, g$ )

---


```
1: if  $g$  has exactly one fanout then
2:    $h =$  fanout gate of  $g$ ;
3:   if none of the inputs of  $h$  has the value of  $X$  then
4:     backtrack;
5:   end if
6: else { $g$  has more than one fanout}
7:    $h =$  pick one fanout gate of  $g$  that is unjustified;
8: end if
9: if gate type of  $h ==$  AND gate then
10:  for all inputs,  $j$ , of  $h$ , such that  $j \neq g$  do
11:    if the value on  $j == X$  then
12:      JustifyFanoutFree( $C, j, 1$ );
13:    end if
14:  end for
15: else if gate type of  $h ==$  OR gate then
16:  for all inputs,  $j$ , of  $h$ , such that  $j \neq g$  do
17:    if the value on  $j == X$  then
18:      JustifyFanoutFree( $C, j, 0$ );
19:    end if
20:  end for
21: else if gate type of  $h == \dots$  gate then
22:   ...
23: end if
24: PropagateFanoutFree( $C, h$ );
```

---
 
# Justify Function, Decisions

---


- ▶ Example circuit  $C$ , fault  $g/1$ .
- ▶ For justification  $g=0$ , either  $a = 0$  or  $f = 0$  can be selected.
- ▶ ATPG should make a decision.
- ▶ **Testability measures** can be used as a guide to make good decisions ( $a = 0$  should be better than  $f = 0$ )


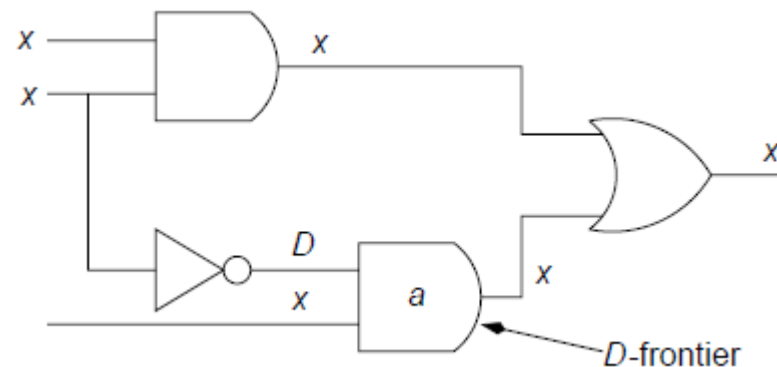
## *D* Algorithm (Roth)

---


- ▶ The first complete ATPG algorithm -> if the fault is detectable, *D* algorithm will find a test vector.
- ▶ *D* or *D'* of the target fault is propagated to PO.
- ▶ ***D*-frontier**: all gates whose output value is *x* and fault-effect is at one or more of its inputs.
- ▶ Example of *D*-frontier with one gate:


 
## *D* Algorithm (Roth)

---


- ▶ If the *D*-frontier is empty, the fault can no longer be detected.
- ▶ Example of *D*-frontier with two gates:


 
# *J*-Frontier

---


- ▶ ***J*-frontier**: all gates whose output values are known (any value in 5-valued logic) but they are not yet justified by its inputs.
- ▶ Example of *J*-frontier:


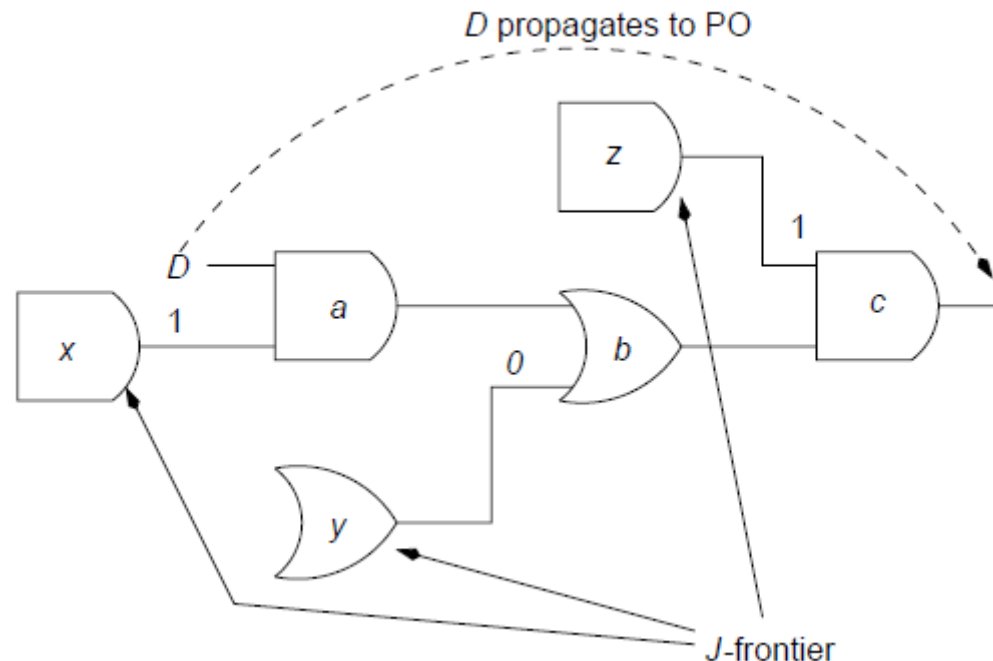
## D Algorithm, Example

---

- ▶ Propagation routine will set all side inputs of the path  $a \rightarrow b \rightarrow c$  to propagate the signal  $D$  to PO.
- ▶ These side input gates  $x$ ,  $y$ ,  $z$ , form the  $J$ -frontier as they are not yet justified.





# *D* Algorithm, Pseudo-Code

---

- ▶ The overall procedure for the *D* algorithm is:

---

**Algorithm 5** *D*-Algorithm(*C*, *f*)

---

```
1: initialize all gates to don't-cares;
2: set a fault-effect (D or  $\bar{D}$ ) on line with fault f and insert it to the D-frontier;
3: J-frontier =  $\phi$ ;
4: result = D-Alg-Recursion(C);
5: if result == success then
6:   print out values at the primary inputs;
7: else
8:   print fault f is untestable;
9: end if
```

---

# D Algorithm, D-Alg-Recursion

---

---

**Alg** Algorithm 6 D-Alg-Recursion(*C*)

---


```
1 1: if there is a conflict in any assignment or D-frontier is  $\emptyset$  then
2 2:   return failure;
3 3: end if
4 4: /* first propagate the fault-effect to a PO */
5 5: if no fault-effect has reached a PO then
6 6:   while not all gates in D-frontier has been tried do
7 7:     g = a gate in D-frontier that has not been tried;
8 8:     set all unassigned inputs of g to non-controlling value and add them to the J-frontier;
9 9:     result = D-Alg-Recursion(C);
10 10:    if result == success then
11 11:      return (success);
12 12:    end if
13 13:  end while
14 14:  return (failure);
15 15: end if {fault-effect has reached at least one PO}
16 16: if J-frontier is  $\emptyset$  then
17 17:   return (success);
18 18: end if
19 19: g = a gate in J-frontier;
20 20: while g has not been justified do
21 21:   j = an unassigned input of g;
22 22:   set j = 1 and insert j = 1 to J-frontier;
23 23:   result = D-Alg-Recursion(C);
24 24:   if result == success then
25 25:     return (success);
26 26:   else try the other assignment
27 27:     set j = 0;
28 28:   end if
29 29: end while
30 30: return(failure);
```

---
 
## *D* Algorithm, Detecting Conflicts

---



- ▶ If there are any conflicts, they should be detected as soon as possible.
- ▶ Example: justifying  $a = 1$  and  $b = 0$  is not possible.
- ▶ Detecting such conflicts helps to avoid future backtracks.


  
# D Algorithm, Examples

---


- ▶ Consider faults  $f/0$  and  $f/1$  in the sample circuit.


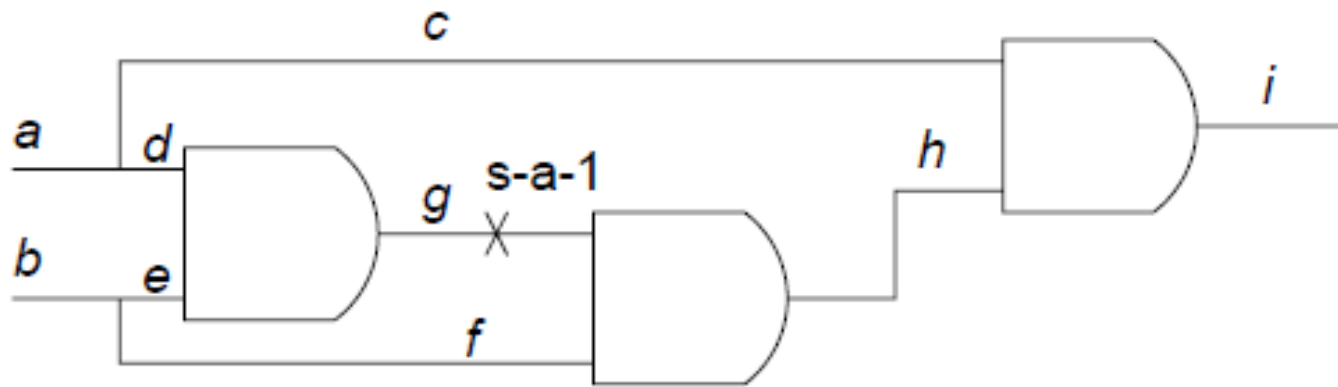
## D Algorithm, Examples

---

- ▶ Consider fault  $g/1$  in the sample circuit.



# PODEM

---

- ▶ In  $D$  algorithm, decisions can be made at every node
- ▶ However, the final result of every test generation step is the test vector – signals at PI.
- ▶ Number of PIs is generally much fewer than number of nodes in the circuits -> decisions are restricted only to PIs.

# PODEM – Pseudo Code

---

- ▶ The overall procedure for the PODEM algorithm is:

---

## Algorithm 7 PODEM( $C, f$ )

---

```
1: initialize all gates to don't-cares;  
2:  $D$ -frontier =  $\emptyset$ ;  
3: result = PODEM-Recursion( $C$ );  
4: if result == success then  
5:   print out values at the primary inputs;  
6: else  
7:   print fault  $f$  is untestable;  
8: end if
```

---

# PODEM – PODEM-Recursion

---

---

**Algorithm 8** PODEM-Recursion( $C$ )

---

```
1: if fault-effect is observed at a PO then
2:   return (success);
3: end if
4:  $(g, v) = \text{getObjective}(C)$ ;
5:  $(p_i, u) = \text{backtrace}(g, v)$ ;
6:  $\text{logicSimulate\_and\_imply}(p_i, u)$ ;
7: result = PODEM-Recursion( $C$ );
8: if result == success then
9:   return(success);
10: end if
11: /* backtrack */
12:  $\text{logicSimulate\_and\_imply}(p_i, \bar{u})$ ;
13: result = PODEM-Recursion( $C$ );
14: if result == success then
15:   return(success);
16: end if
17: /* bad decision made at an earlier step, reset  $p_i$  */
18:  $\text{logicSimulate\_and\_imply}(p_i, x)$ ;
19: return(failure);
```

---



# PODEM – getObjective

---

---

## Algorithm 9 getObjective( $C$ )

---

```
1: if fault is not excited then  
2:   return  $(g, \bar{v})$ ;  
3: end if  
4:  $d =$  a gate in  $D$ -frontier;  
5:  $g =$  an input of  $d$  whose value is  $x$ ;  
6:  $v =$  non-controlling value of  $d$ ;  
7: return  $(g, v)$ ;
```

---

# PODEM – Backtrace

---

---

## Algorithm 10 backtrace( $C$ )


---

```
1:  $i = g$ ;  
2: num_inversion = 0;  
3: while  $i \neq$  primary input do  
4:    $i =$  an input of  $i$  whose value is  $x$ ;  
5:   if  $i$  is an inverted gate type then  
6:     num_inversion++;  
7:   end if  
8: end while  
9: if num_inversion == odd then  
10:   $v = \bar{v}$ ;  
11: end if  
12: return( $i, v$ );
```

---

# PODEM – Example

- ▶ Consider fault  $f/0$ :

 


<b>getObjective()</b>	<b>backtrace()</b>	<b>logicSim()</b>	<b>D-frontier</b>
$f = 1$	$c = 0$	$d = 0, f = D,$ $e = 0, h = 0$	$g$
$a = 1$	$a = 1$	$g = D, z = D$	$f/0$ detected


Test vector 1X0

# PODEM – Example

- ▶ Consider fault  $b/0$ :

 


<code>getObjective()</code>	<code>backtrace()</code>	<code>logicSim()</code>	<i>D</i> -frontier
$b = 1$	$a = 0$	$b = 1, c = 0, d = 0$	$\emptyset$
$a = 1$ (reversal)	—	$b = 0, c = 1, d = 0$	$\emptyset$

 

Fault  $b/0$  is undetectable.

# PODEM – Example

- ▶ Consider fault  $g/1$ :

 

<b>getObjective()</b>	<b>backtrace()</b>	<b>logicSim()</b>	<b>D-frontier</b>
$g = 0$	$a = 0$	$g = D, c = 0$ $d = 0, i = 0$	$h$ (but no X-path to PO)
$a = 1$ (reversal)	—	$c = 1, d = 1$	$\emptyset$

Fault  $g/1$  is undetectable.

# FAN


---

- ▶ PODEM can still make an excessive number of decisions.
- ▶ FAN (Fanout-Oriented TG) algorithm improves PODEM by reducing the number of decision points.
- ▶ FAN identifies headlines in the circuit, which are the output signals of fanout-free regions -> any value assignment on the headline can always be justified by its fanin cone.
- ▶ Backtrace function stops at PI (as in PODEM) or at headlines, thus reducing the number of decision points.
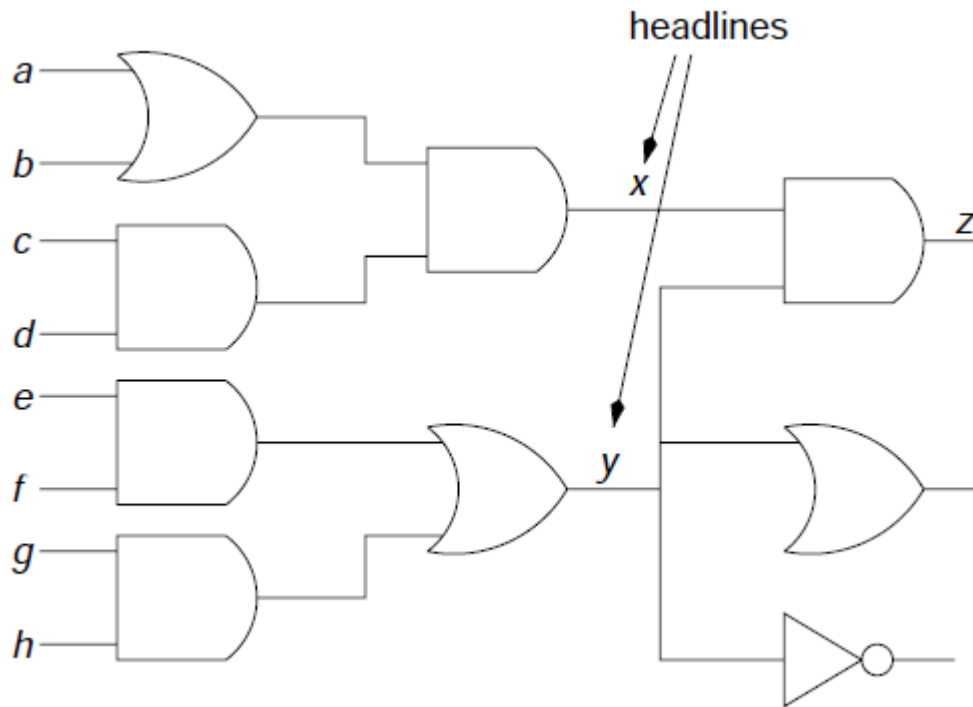
# FAN - Example

---


- ▶ Consider objective  $z = 1$ .
- ▶ PODEM:  $a=1, c=1, d=1, e=1, f=1$
- ▶ FAN:  $x=1, y=1$


 
# FAN – Multiple Objectives

---

- ▶ FAN considers simultaneously multiple objectives.
- ▶ Justify  $k=0$ 
  - ▶ Selecting  $b=0$  causes a conflict later with objective  $m=1$





 
# Logic Implications

---



- ▶ Logic implications capture the effect of assigning logic values on other gates in order to make better decisions.
- ▶ Example:



- ▶ They can be divided into
  - ▶ Static logic implications
  - ▶ Dynamic logic implications
 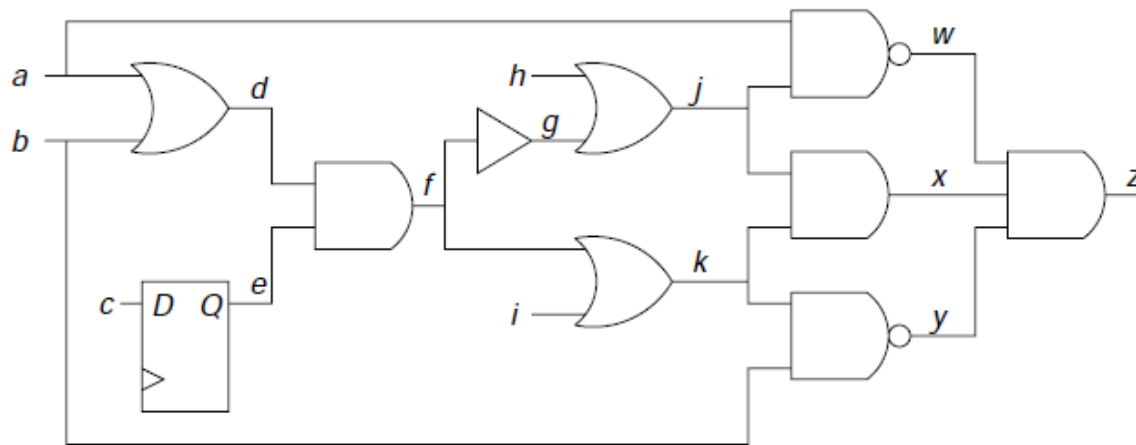
# Static Logic Implications


- ▶ Direct implications
- ▶ Example, implication of logic value  $f = 1$ .


 
# Static Logic Implications

---


- ▶ Indirect implications
- ▶ Can be computed by performing logic simulation on the current set of logic implications.
- ▶ Example, implication of logic value  $f = 1$ .


 
# Static Logic Implications

---


- ▶ Extended backward implications
- ▶ Can be computed by performing logic simulation on the current set of logic implications.
- ▶ Example, implication of logic value  $f = 1$ .


 
# Dynamic Logic Implications

---


- ▶ Static logic implications are computed once for the entire circuit, dynamic implications are performed during the ATPG process.
- ▶ Example, implication of logic value for  $z = 0$  by  $c = 1$ .
- ▶  $d=0 \rightarrow \{a=0, b=0\}$     $e=0 \rightarrow \{b=0\}$
- ▶ Dynamic implication for  $z = 0$  by  $c = 1 \rightarrow \{b=0\}$


 
# Dynamic Logic Implications

---


- ▶ Dynamic logic implications can be used also for signals with fault-effect.
- ▶ Example, fault signal is on node  $b$ . In order to propagate fault signal to PO  $z$ , necessary condition is  $f=1$ .


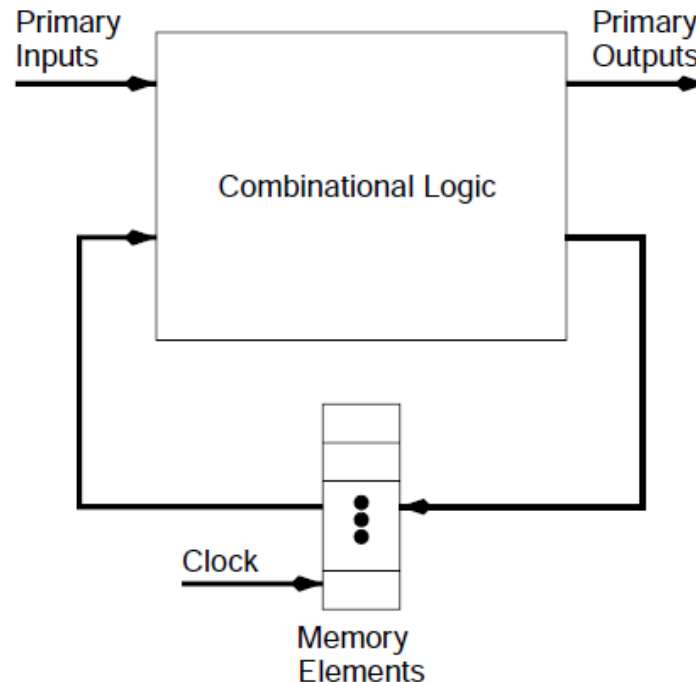
# Test Generation for Sequential Circuits


---

- ▶ One test vector may be insufficient to detect the target fault since the excitation and propagation conditions may necessitate some of the flip-flop values.
- ▶ General model of sequential circuit:


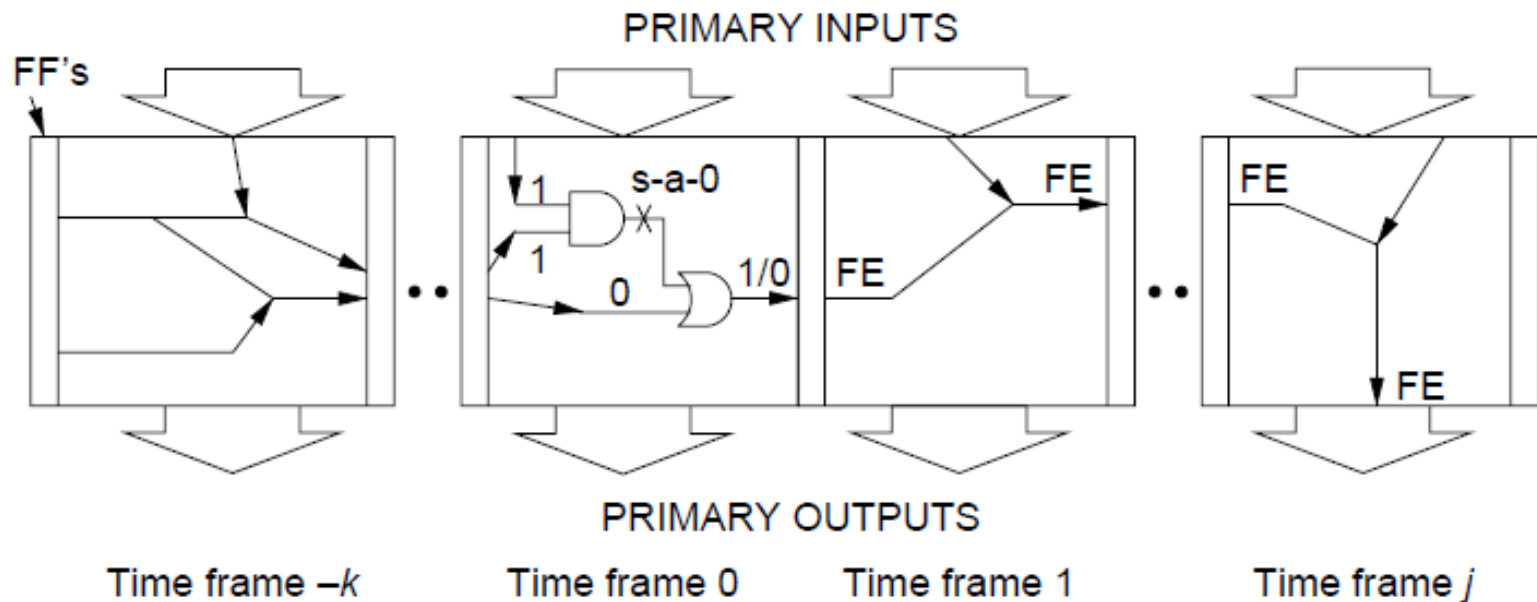
# Time Frame Expansion

- ▶ Method for transforming sequential circuit into combinational circuit over several time frames (iterative logic array).
- ▶ Target fault is present in every time frame.





 
## 5-Valued Algebra is Insufficient

---


- ▶ Consider the target fault  $b/0$ .
- ▶ Values  $a=1/0$  or  $a=1/1$  propagates the fault signal over the AND gate.
- ▶ This can be written as  $a=1/X$ .


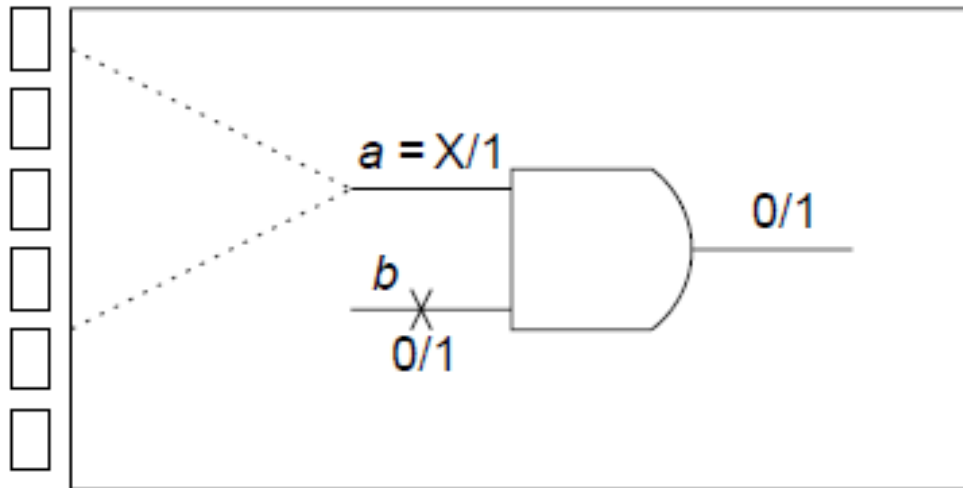
## 5-Valued Algebra is Insufficient

---


- ▶ Consider the target fault  $b/1$ .
- ▶ Values  $a=1/1$  or  $a=0/1$  propagates the fault signal over the AND gate.
- ▶ This can be written as  $a=X/1$ .
- ▶ Additional values are therefore:  **$1/X$ ,  $0/X$ ,  $X/1$ ,  $X/0$** , all together **9 values (9-Valued Algebra)**


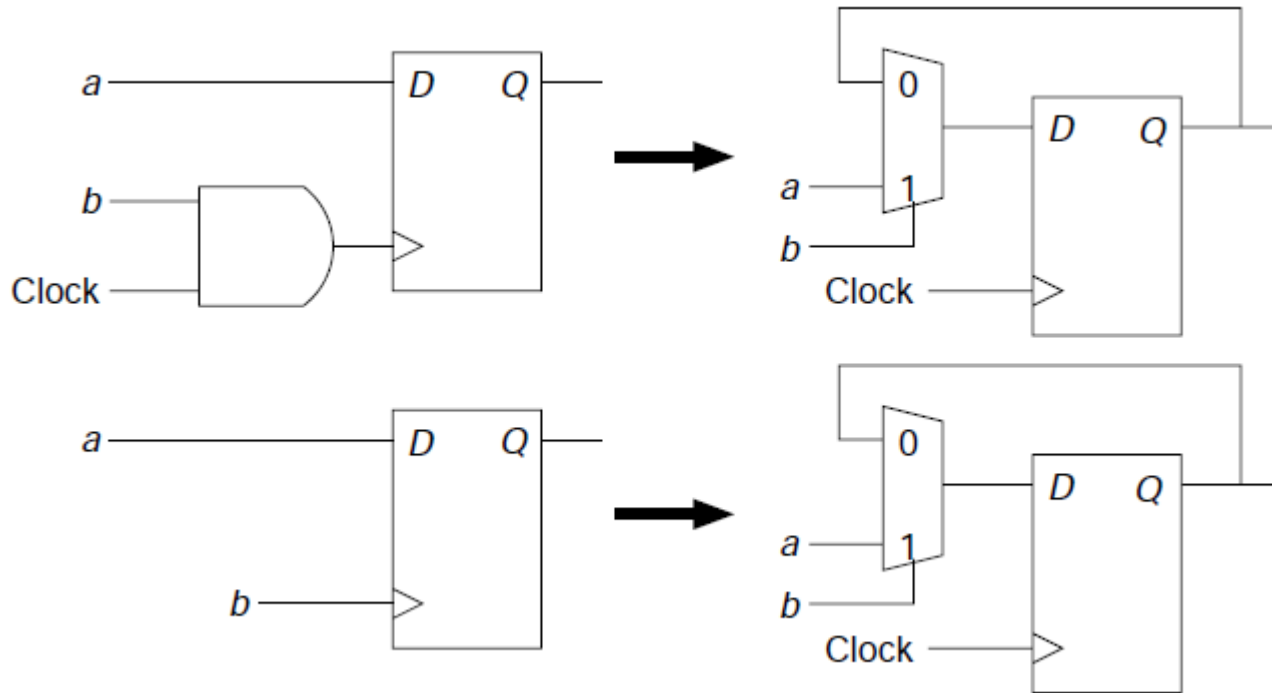
# Gated Clocks

---


- ▶ Gated clocks are used for power saving.
- ▶ Transformation are used to ease ATPG process.


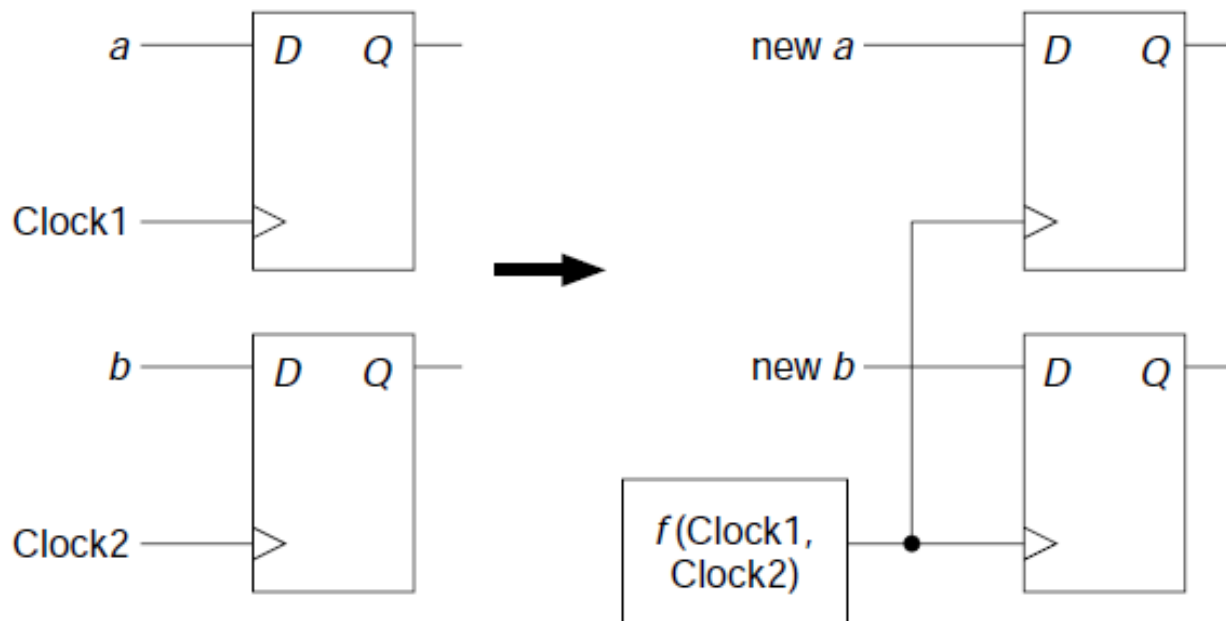
# Multiple Clocks

---

- ▶ Multiple clocks benefit performance and power as circuit blocks are partitioned to different clock domains.
- ▶ Example of transformation:



# Other issues in Deterministic TPG

---

- ▶ Untestable fault identification
- ▶ Multiple-line conflict analysis
- ▶ Genetic algorithms
- ▶ Testing for bridging and delay faults
- ▶ Testing of acyclic sequential circuits
- ▶ Using testing for logic and power optimization