

# High-Level FPGA Design

## Lab 1: Averaging Filter RTL Design

**Audience:** Digital designers familiar with HDL, simulation, synthesis, timing

**Duration:** 90–120 minutes

**Purpose:** Establish baseline RTL reference for later conversion/comparison to HLS

### 1. Learning Objectives

By the end of Lab 1, participants will be able to:

- Implement a **streaming averaging filter in RTL**
- Understand **latency, throughput, and resource usage** in a concrete design
- Express the design in **clock-by-clock behavior**, preparing for HLS comparison
- Generate **post-synthesis metrics** that will later be compared to HLS results

### 2. Problem Statement

#### Functional Specification

Design a **moving average filter**:

$$y[n] = \frac{1}{N} \sum_{i=0}^{N-1} x[n - i]$$

Where:

- N = 8 samples (power-of-two on purpose)
- Input: signed 16-bit samples, parameter DATAW = 16
- Output: signed 16-bit rounded result
- Basic streaming interface: in\_valid, out\_valid

#### Interface (explicit RTL contract)

```

module lab1_avg #(
    parameter int N = 8,
    parameter int DATAW = 16
) (
    input logic      clk;
    input logic      rst;
    input logic      in_valid;
    input logic signed [DATAW-1:0] in_data;

    output logic      out_valid;
    output logic signed [DATAW-1:0] out_data
);

```

### 3. Suggested Architecture (RTL-friendly)

#### Reference Architecture

- Shift register (N=8) for sample history
- Accumulator width:  $16 + \log_2(8) = 19$  bits
- Division by 8 = right shift by 3 bits
- Two optimized versions: adder tree and running sum ( $\text{sum\_next} = \text{sum} + \text{new\_sample} - \text{oldest\_sample}$ )

#### Key RTL Concepts

- Word growth
- Pipeline latency
- Explicit control of registers
- Clock enable via `in_valid`

### 4. Step-by-Step Instructions

#### Step 1: Create Vivado Project

- Target Board: Red Pitaya or Device `xc7z010clg400-1`
- Add Sources, Add design sources, Add Files, [lab1\\_avg.sv](#)
- Add Sources, Add Constraints, [constraints.xdc](#)

#### Step 2: Declare Signals and Describe Shift Register


- Declare array for shift register `shift_r[N]`
- Describe data shifting in `always_ff` block, `@(posedge clk)` and when `in_valid`
  - Reset all registers and output when `rst` asserted
- For the first test let `out_data = shift_r(N-1)`

```

for (i = N-1; i > 0; i--) begin
    shift_r[i] <= shift_r[i-1];
end
shift_r[0] <= in_data;
out_data <= shift_r[N-1]; // for the first test


```

 - Perform RTL Analysis, Open Elaborated Design Schematic
  - You should see 8 registers and `out_data` register



- Run Simulation, Run Behavioral Simulation
- Use small TCL script for setting inputs (source ./src\_lab1/sim.tcl)
 
```
add_force {/lab1_avg/clk} -radix bin {1 0ns} {0 50ns} -repeat_every 100ns
add_force {/lab1_avg/rst} -radix bin {1 0ns}
add_force {/lab1_avg/in_valid} -radix bin {1 0ns}
add_force {/lab1_avg/in_data} -radix dec {5 0ns}
run 100 ns
add_force {/lab1_avg/rst} -radix bin {0 0ns}
run 1000 ns
```




### Step 3: Compute average

- Declare sum, use parameter to specify width  
**localparam int SUMW = DATAW + \$clog2(N);**
- Add combinational block with for loop to describe adder

```
always_comb begin
    sum = '0;
    for (j = 0; j < N; j++) sum = sum + shift_r[j];
end
```

- Assign sum divided by 8 (right shift) to the **out\_data**
- How to parametrize right shift amount?
- Check on simulation. What are expected results with this input sequence?

in_data	0	5	5	5	5	5	5	5	5
out_data	0	0	1						

 

#### Step 4: Testbench and interface

Testbench will be used for verification and automatic latency measurement.

**Latency** is number of clock cycles between the cycle where an input is *accepted* and the cycle where the *corresponding output* is asserted *valid*.

- Add Sources, Add Simulation Sources, [tb\\_avg.sv](#)
- The testbench performs 3 tests: impulse input, constant input and ramp
- Initial reset and toggling in\_valid
- Now you should upgrade control interface to provide out\_valid and uncomment automatic checking of out\_data
- option 1: **out\_valid** is asserted following **in\_valid** (1 cycle latency). The average filtering result should be computed with combinational logic.


```

end else if (in_valid) begin
    ...
    out_valid <= 1;
end

```

- option 2: The result is stored in register (better circuit performance) and **out\_valid** has additional clock cycle delay. Consider this option for your design.
 
#### Simulation with **out\_valid**, 2 cycle latency



Adding one register increases latency to 2 cycles, which is not a problem in typical signal processing design. But multi-cycle computation can add requirement to send the data slowly (pause between in\_valid cycles), unless the circuit is implemented with pipeline.


**Fully pipelined** circuits can accept new input at each clock cycle and produce valid results with fixed delay corresponding to the latency.

**Initiation Interval (II)** is minimum number of cycles between accepting consecutive inputs. Fully pipelined circuits have initiation interval  $II = 1$ .

**Throughput** is the *rate of completed results* produced by the design in *steady state*, given in results per second or per cycle. For optimal case, after pipeline fill, throughput =  $1 / II$ .

- Comment automatic checking in the testbench, which will reduce pause between input valid to 0 cycles and check operation of your circuit.
- How to create averaging filter with one cycle pipeline?

 Checking pipeline performance, latency = 2,  $II = 1$



### Step 5: Evaluate implemented design performance


- Run Synthesis, Open Synthesized Design
- Check Utilization
- Check Data Path Delay with TCL command

```
report_timing -delay_type max -max_paths 1
```


- Run Implementation
- Report timing and read Worst Negative Slack (WNS)
  - Note: min clock period = 8 ns – WNS
- Compute max clock frequency

FPGA Utilization	LUT	FF
Timing	Delay	Freq

 - What is a problem of long sequence of adders considering performance?



- Adder tree would be better solution...

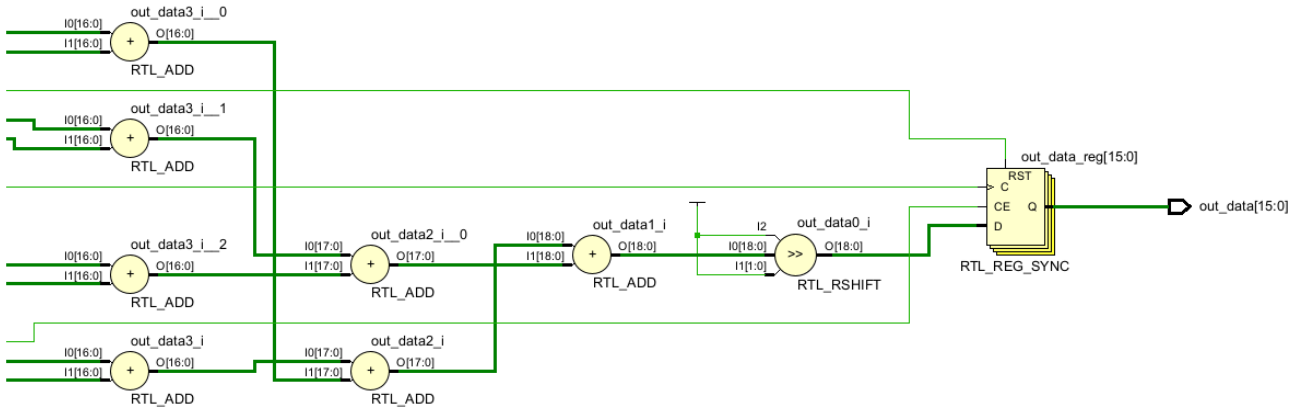

### Step 6: Optimize circuit

- Optimal implementation of the averaging filter utilizes **running sum**
- Value of sum should be stored in a register  
 $sum \leq sum + in\_data - shift\_r[N-1];$
- Simulate circuit to check operation
- Run Synthesis and Implementation
- Check utilization and timing performance

8 adders: LUT 75, FF 144, 6.3 ns, 139 MHz

tree: LUT 116, FF 144, 5.822ns, 159 MHz

Running: LUT 44, FF 74, Data Path Delay 3.402ns, 276 MHz

### Step 7: Check FPGA Primitive Usage

- Compare synthesis Utilization for N=8 and N=1024
- Synthesis maps shift register to FFs or SRL cells

Primitive	N=8	N=1024	Category
FDRE	76	1099	Flop & Latch
SRLC32E	20	512	Distributed Memory
LUT2	19	27	LUT
IBUF	17	19	IO
OBUF	16	17	IO
LUT4	16	16	LUT
LUT3	16	16	LUT
CARRY4	5	7	CarryLogic
BUFG	1	1	Clock

- Consider implementation of data storage with RAM and pointers

```
// 1. Subtract the oldest sample and add the newest
// Update running sum: NewSum = OldSum + NewSample - OutgoingSample
sum <= sum + in_data - ram[ptr];

// 2. Overwrite the oldest sample in the circular buffer (BRAM)
ram[ptr] <= in_data;

// 3. Update pointer
ptr <= ptr + 1;
```

## 5. \*Optional Stretch Tasks

- Implement rounded division by power of 2
- Add integer divider if N is not power of 2
  - Check circuit timing
- Switch to saturation arithmetic
  - Use smaller sum register and saturation instead of overflow
- Force DSP usage and observe mapping