



Laboratorij za načrtovanje integriranih vezij

Univerza *v Ljubljani*  
Fakulteta *za elektrotehniko*



## Red Pitaya – elektronske orgle


DES 2017/18 - razvoj vgrajenega sistema

# Elektronske orgle na vezju FPGA

---

- ▶ načrtovanje generatorja tonov
- ▶ vmesnik za tipkovnico (PS/2)
- ▶ grafika za prikaz na zaslonu VGA

Altera DE0 Nano

 


# Generator tonov v digitalnem vezju

## 1. Delilnik frekvence

- ▶ naredimo števec po modulu  $M$ : števec šteje od 0 do  $M-1$
- ▶ izhodna frekvenca je določena s periodo obračanja števca, za izhod uporabimo najvišji bit ali pa doseg modula štetja
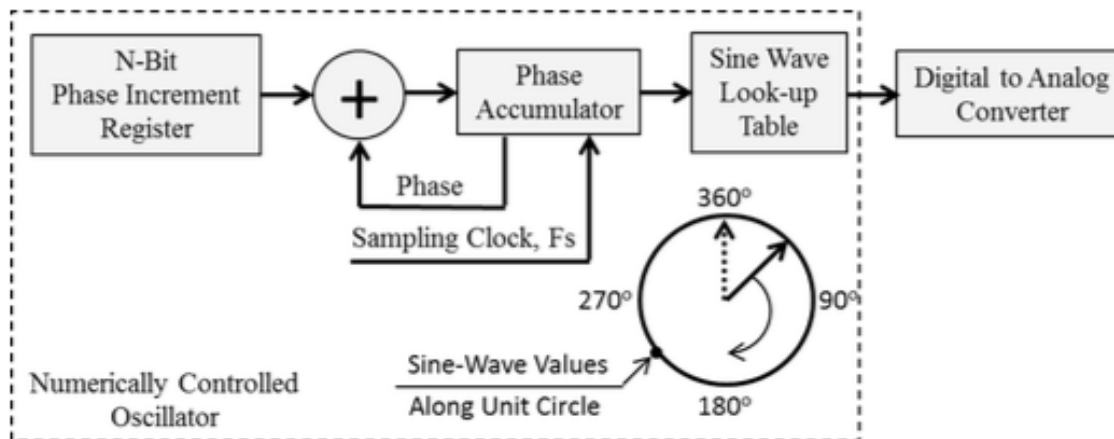
## 2. Numerično krmiljen oscilator

- ▶ naredimo  $n$ -bitni števec, ki se povečuje za korak  $\Delta f$
- ▶ izhodna frekvenca je določena s periodo obračanja števca, uporabimo najvišji(e) bit(e) števca



```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;
USE ieee.math_real.all;

entity rom is
  port (
    adr : in unsigned(5 downto 0);
    data : out signed(7 downto 0)
  );
end rom;

architecture Behavioral of rom is
  constant romsize: integer := 64; -- stevilo elementov sinusne tabele

  type sintab is array(0 to romsize-1) of signed(7 downto 0);
  signal sinrom: sintab;
begin

  -- generator vsebine sinusne tabele
  g: for i in 0 to romsize-1 generate
    constant sinval: signed (7 downto 0) :=
to_signed(integer(127.0*sin(real(i)*2.0*math_pi/real(romsize))),8);
  begin
    sinrom(i) <= sinval;
  end generate;

  -- tabela kot pomnilnik ROM
  data <= sinrom(to_integer(adr));

end Behavioral;

```

# Primerjava delilnika in numeričnega oscilatorja


---

Vhod: 50 Hz, izhod: 4 Hz (razmerje 12.5)

▶ delilnik: 12 => 4.16 Hz ali 13 => 3.84 Hz



▶ NCO: 6-bit,  $\Delta f=5$  => 3.906 Hz

10-bit,  $\Delta f=82$  => 4.004 Hz

 
  
# Vmesnik PS/2


- ▶ Zaporedni vmesnik za branje tipkovnice
  - ▶ tipkam so dodeljene scan kode




PS/2

 1. KBD Clock
2. GND
3. KBD Data
4. N/C
5. +5V (VCC)
6. N/C


- ▶ zaporedje: start ('0'), podatkovni biti od LSB do MSB, liha pariteta in stop ('1')



# Sinhrono zaznavanje PS/2 prehodov

 

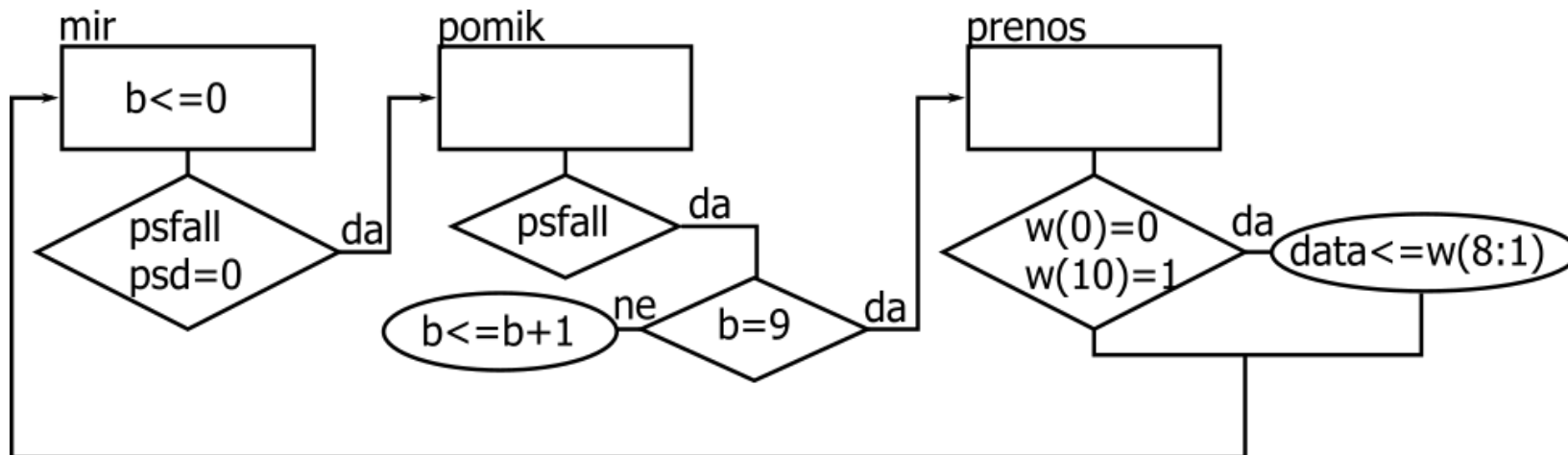- ▶ Algoritmični sekvenčni stroj za sprejem podatkov



```

stim_proc: process
  procedure oddaj (D : std_logic_vector(7 downto 0)) is
  begin
    psdata <= '0'; -- Start bit
    wait for (PS2Period / 2);
    psclk <= '0'; wait for (PS2Period / 2);
    psclk <= '1';

    for i in 0 to 7 loop -- Data Bits
      psdata <= D(i);
      wait for (PS2Period / 2);
      psclk <= '0'; wait for (PS2Period / 2);
      psclk <= '1';
    end loop;

    psdata <= odd(D); -- Odd Parity bit
    wait for (PS2Period / 2);
    psclk <= '0'; wait for (PS2Period / 2);
    psclk <= '1';

    psdata <= '1'; -- Stop bit
    wait for (PS2Period / 2);
    psclk <= '0'; wait for (PS2Period / 2);
    psclk <= '1';
    wait for (PS2Period * 3);
  end procedure oddaj;

begin
  psdata <= '1';
  psclk <= '1';
  wait for (PS2Period * 3);

  oddaj(x"F0");

```



# Primer opisa komponente IP: I2C vmesnik

## Opis namena in lastnosti komponente

The I<sup>2</sup>C is a two-wire, bi-directional serial bus, which provides simple and efficient method of data transmission over short distance, between many devices. The DI2CM core provides an interface between a microprocessor / microcontroller and an I<sup>2</sup>C bus. It can work as a master transmitter or a master receiver - depending on a working mode determined by the microprocessor / microcontroller.

### KEY FEATURES

- Conforms to v.4.0 of the I<sup>2</sup>C specification
- Master operation
  - Master transmitter
  - Master receiver
- Support for all transmission speeds
  - Standard (up to 100 kb/s)
  - Fast (up to 400 kb/s)

### DELIVERABLES

- ◆ Source code:
  - VHDL Source Code
  - Encrypted, or plain text EDIF
- ◆ VHDL & VERILOG test bench environment

## Rezultati sinteze (lastnosti vezja v izbrani tehnologiji)

Family	Device	Speed grade	LUT	Slice	F <sub>max</sub>
SPARTAN-3	xc3s50	-5	271	194	161 MHz
SPARTAN-3E	xc3s100e	-5	264	190	162 MHz
SPARTAN-6	xc6slx4	-3	173	75	270 MHz

[https://dcd.pl/workspace/documentation/xil/di2cm\\_ds.pdf](https://dcd.pl/workspace/documentation/xil/di2cm_ds.pdf)

## Blokovna shema in opis gradnikov

**Control Logic** – Manages execution of all commands sent via interface. Synchronizes internal data flow.

**Shift Register** – Controls SDA line, performs data and address shifts, during the data transmission and reception.

**Control Register** – Contains five control bits, used for performing all types of I<sup>2</sup>C Bus transmissions.

**Status Register** – Contains seven status bits that indicate state of the I<sup>2</sup>C Bus and the DI2CM core.

**Clock Generator** – Performs generation of the serial clock.

**Input Filter** – Performs spike filtering.

**Clock Synchronization** – Performs clock synchronization.

**Arbitration Logic** – Performs arbitration during operations in multi-master systems.

**Timer** – Allows operation from a wide range of the input frequencies. It is programmed by the user before transmission and can be reprogrammed to change the SCL frequency.

## Shema in opis priključkov

